
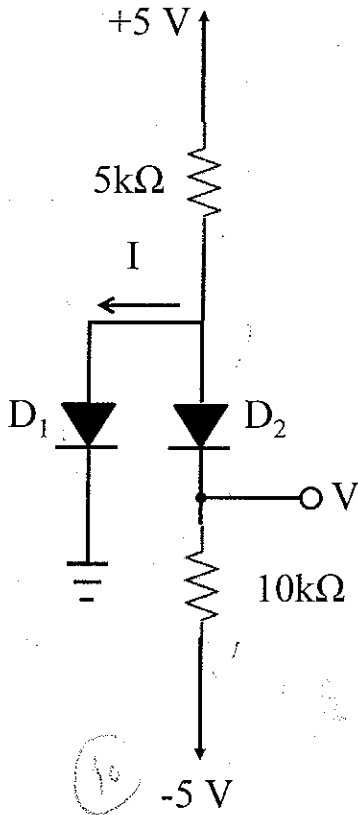


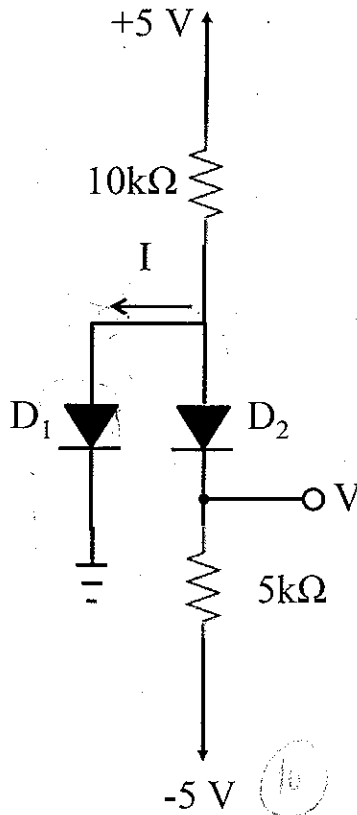Problem 1


Assuming that the diodes in the circuits below are ideal, find the values of the labeled voltages and currents.



(a)




(b)

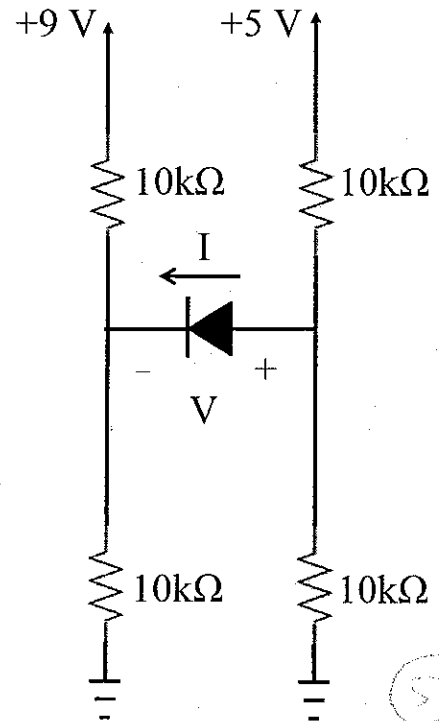


(c)

part a assume D_1 ON D_2 off

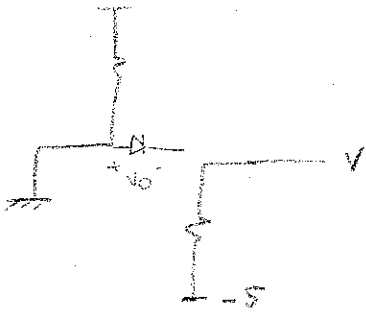

$V_{D2} = -5$ wrong assu

both ON

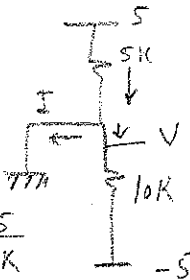

$$V = 0V$$

$$I = \frac{5}{5K} - \frac{0+5}{10K}$$

$$= 1 - 0.5$$

$$I = 0.5mA$$

$$I_{D1} > 0, I_{D2} = 0.5mA > 0$$


(b) assume D_2 ON, D_1 off

$$I = 0$$

$$V = \frac{5 \cdot 5}{15} - \frac{5 \cdot 10}{15} = -\frac{5}{3}V$$

$$V = -1.67V$$


$$V_{D1} = -1.67 < 0$$

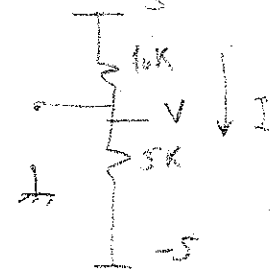

$$I_{D1} = \frac{2}{3}mA > 0$$

© using the.
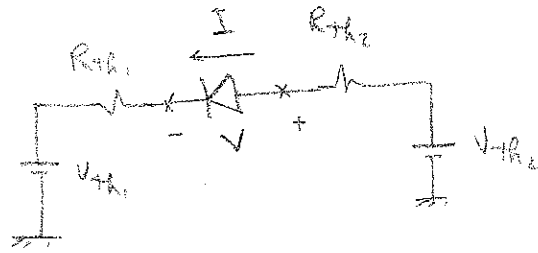
$$R_{th1} = R_{th2} = 10K // 10K \\ = 5K\Omega$$



$$V_{th1} = 9 \frac{10}{10+10} = 4.5V$$

$$V_{th2} = 5 \frac{10}{10+10} = 2.5V$$

$\therefore V_{th2} < V_{th1} \Rightarrow D$ is off


$$I = 0$$

$$V = V_{th2} - V_{th1} = 2.5 - 4.5 = -2V < 0$$

* $V_D < 0$ assumption is verified

Using a 5-V power supply, V_{CC} , the feedback bias circuit in the figure shown below provides $I_C = 1\text{mA}$ and $V_C = 2\text{V}$ for $\beta_F = 90$.

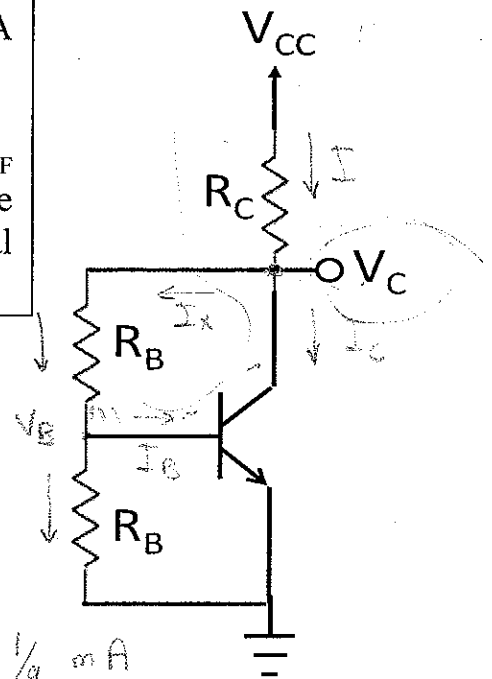- Find R_C and R_B .
- Find V_C and I_C for very large value of β_F (i.e., $I_C \approx I_E$). In which mode does the transistor operate? What is the ideal value of β_F ?



$V_{CE} = 2\text{V} > 0.2$ Q is active

(i)

$$I = \frac{5 - 2\text{V}}{R_C} = \frac{3}{R_C}$$

$$V_{BE} = 0.7\text{V}$$

$$V_B = 0.7\text{V}, \quad I_B = \frac{I_C}{\beta} = \frac{1}{90}\text{mA}$$

KCL at (1).

$$\frac{V_C - V_B}{R_B} = \frac{V_B}{R_B} + I_B$$

$$\frac{1}{R_B} [V_C - 2V_B] = I_B$$

$$R_B = \frac{V_C - 2V_B}{I_B} = 54\text{k}\Omega \quad (5)$$

$$I_x = \frac{V_C - V_B}{R_B} = \frac{2 - 0.7}{54} = \frac{13}{540}\text{mA} = 0.0241\text{mA}$$

$$I = I_C + I_x = 1.0241\text{mA}$$


$$R_C = \frac{V_{CC} - V_C}{I} = \frac{5 - 2}{1.0241} \approx 2.929 \approx 3\text{k}\Omega \quad (5)$$

(ii) if β is large $\therefore I_E \approx I_C$, $I_B = 0$
assume Active

$$V_{BE} = 0.7\text{V}, \quad V_B = 0.7\text{V}$$

$$I_x = \frac{V_B}{R_B} = \frac{0.7}{540}\text{mA} = 0.1296\text{mA}$$
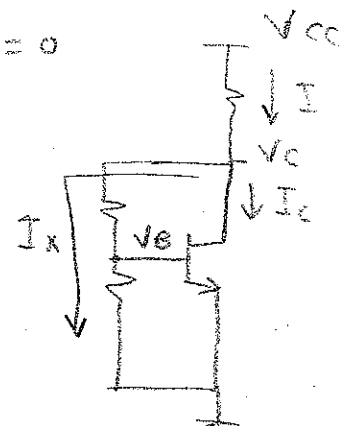
$$V_C = I_x \times 2R_B = 1.4\text{V} \quad (4)$$



$$I = \frac{V_{CC} - V_C}{R_C} = 1.2 \text{ mA} \quad (4)$$

$$I_C = 1.07 \text{ mA} = I_E$$

Check $V_{CE} = 1.4 \text{ V} > 0.2$

Assumption is correct

Q is Active




* For Ideal value of $\beta_F = \infty$ 2



(i)

→ For $V_{in} < 0.7$
 $V_o = 0$

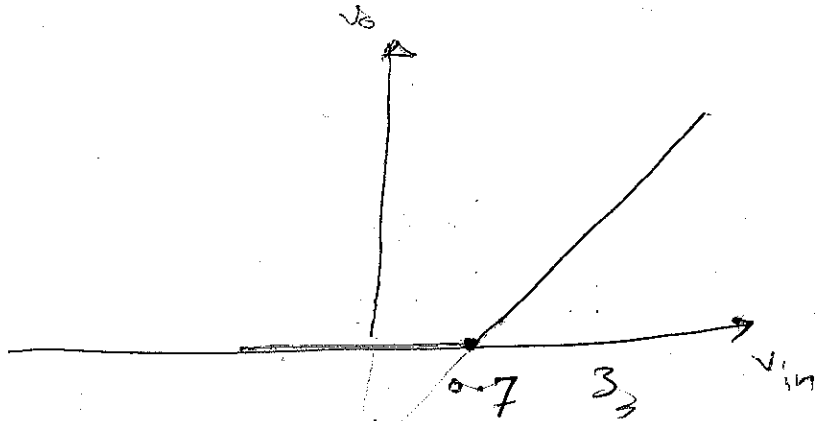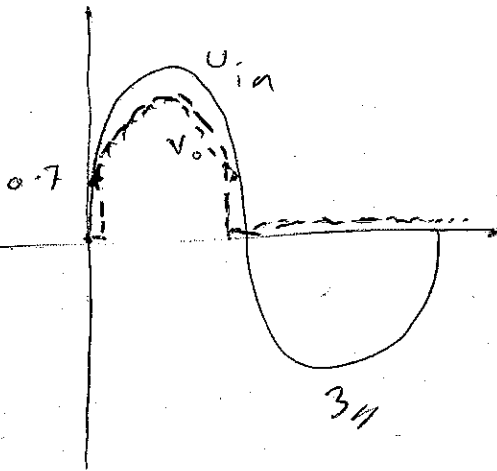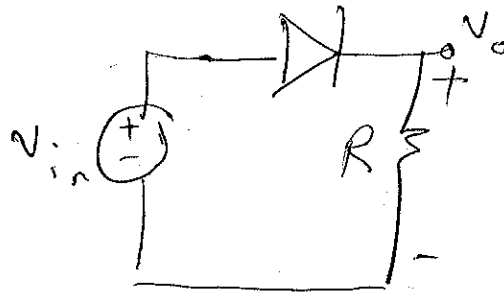→ For $V_{in} > 0.7 \Rightarrow V_o = V_{in} - 0.7$






(ii) → For $V_{in} < 0.7$

$$V_o = V_{in}$$


→ For $V_{in} > 0.7$

$$V_o = 0.7$$

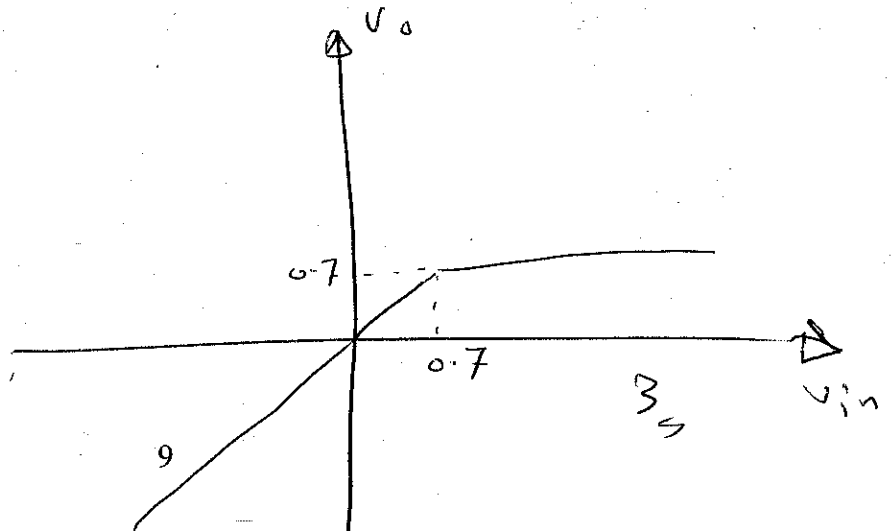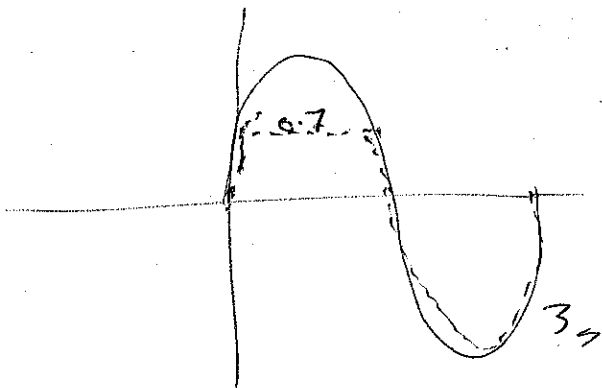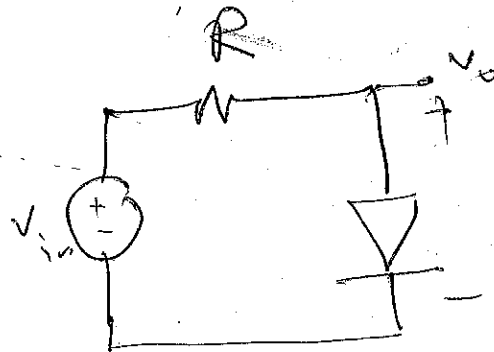


[a]

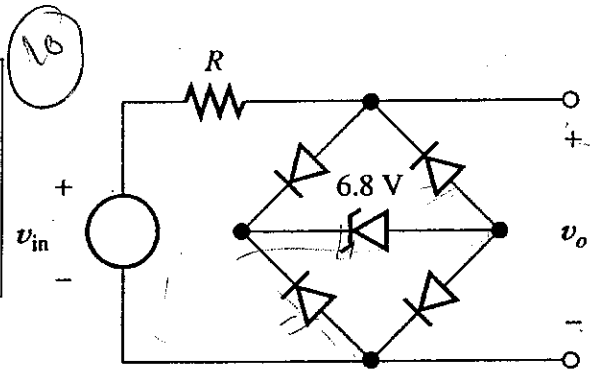Consider the circuit in the figure shown. Allow 0.6V for the forward drops of the diodes. Sketch the transfer characteristics v_o versus v_{in} .



(i) $v_{in} > 0$ $\left\{ \begin{array}{l} v_{in} < 8 \Rightarrow v_o = v_{in} \\ v_{in} > 8 \Rightarrow v_o = 8V \end{array} \right.$

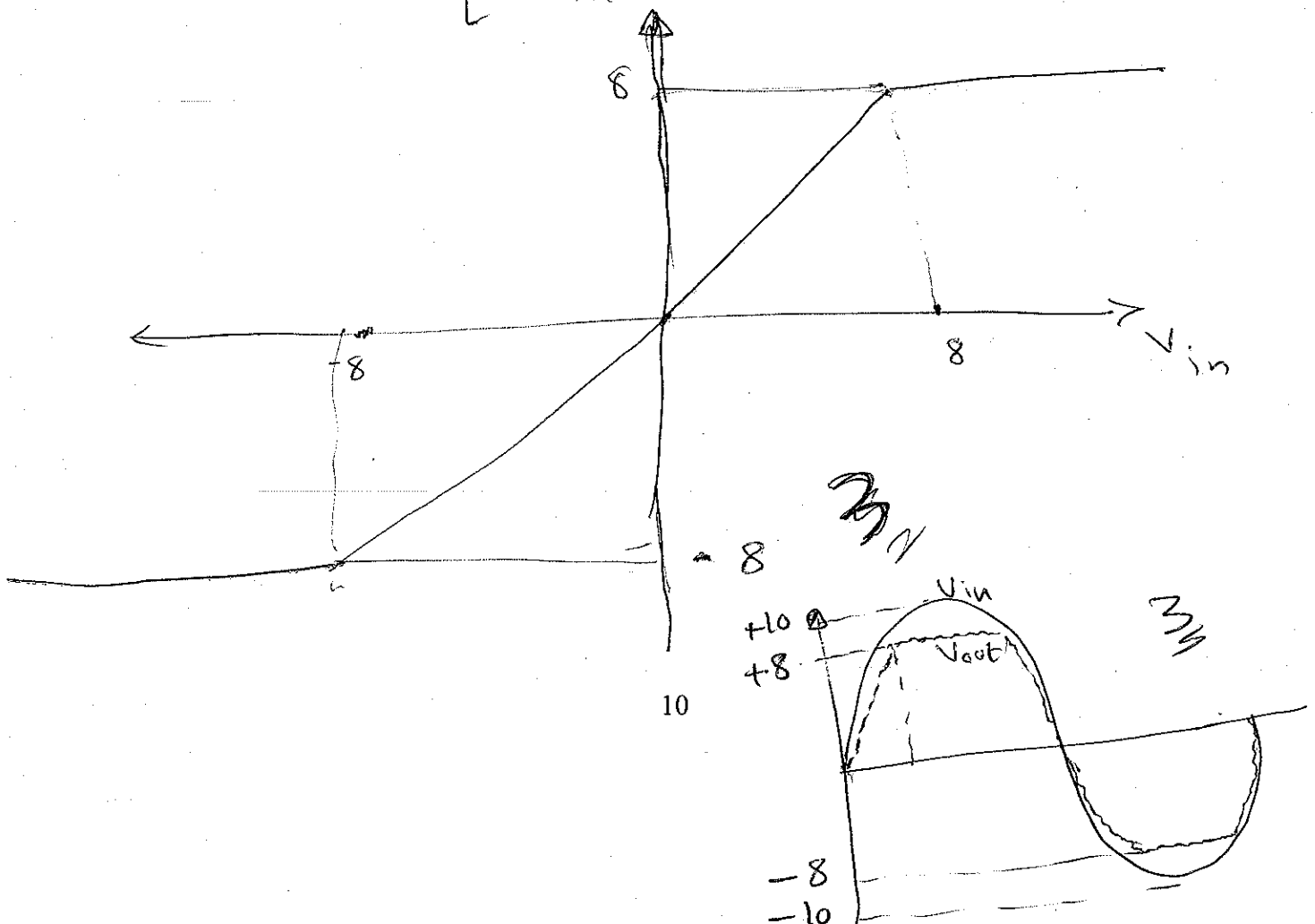(ii) $v_{in} < 0$ $\left\{ \begin{array}{l} v_{in} > -8 \Rightarrow v_o = v_{in} \\ v_{in} < -8 \Rightarrow v_o = -8V \end{array} \right.$



[4][b]

$$\text{[3]} V_B = -0.1 \text{ V}$$

$$V_{BE} = 0.7$$

$$V_B = -0.1$$

$$\therefore V_E = -0.8 \text{ V}$$

$$I_E = \frac{-0.8 - (-9)}{10k} \\ = 0.82 \text{ mA}$$

$$I_B = \frac{0 - (-0.1)}{10k} = 0.01 \text{ mA}$$


$$I_C = I_E - I_B = 0.81 \text{ mA}$$

$$V_C = 9 - 10k(I_E) = 0.9 \text{ V}$$

$$V_{CE} = 0.9 - (-0.8) = 1.7 \text{ V}$$

$V_{CE} > 0.2$ \therefore active.
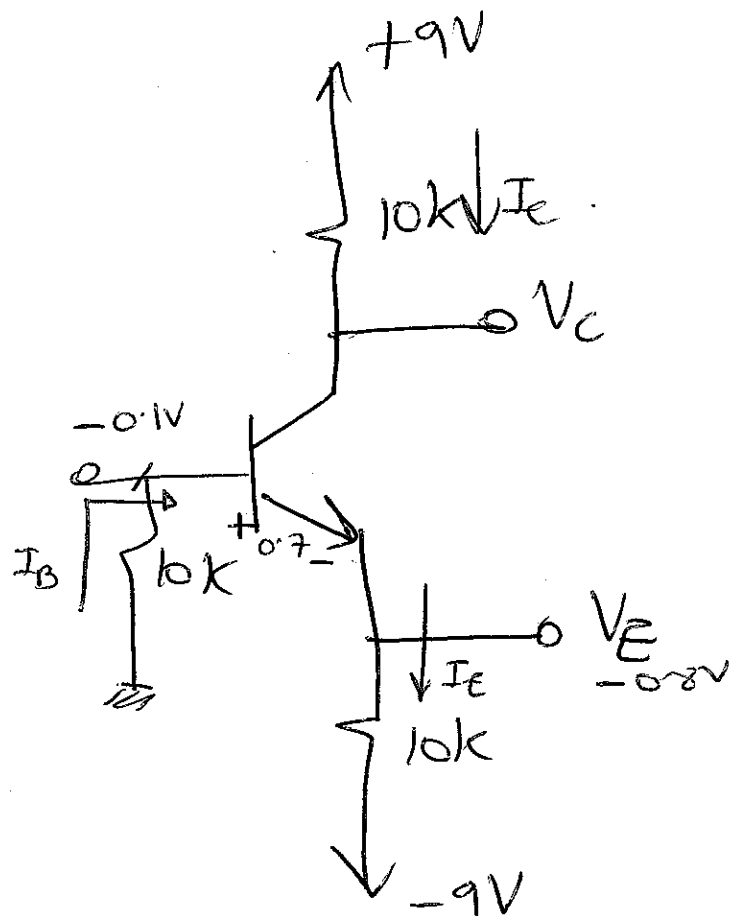
$$\beta = \frac{I_C}{I_B} = \frac{0.81 \text{ mA}}{0.01 \text{ mA}} = 81$$



$$[ii] \beta = \infty$$

$$\therefore I_B = 0, V_B = 0$$

$$V_E = -0.7V$$

$$I_E = \frac{-0.7 - (-9)}{10k} = 0.83mA$$

$$\therefore I_B = 0, \therefore I_E = I_C = 0.83mA$$

$$\begin{aligned} \therefore V_C &= 9 - 10k(0.83mA) \\ &= 9 - 8.3 = 0.7V \end{aligned}$$

$$V_{CE} = 1.4V > 0.2 \quad \therefore \text{active}$$