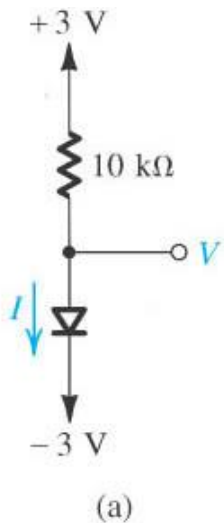



Sheet 2: PN Junctions

Problem 1:


For the following circuits employing ideal diodes, find the labeled currents I and voltages V measured with respect to ground?




(Ans. 0.6 mA, -3V)

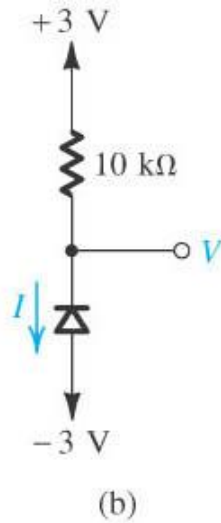

(0mA, 3V)

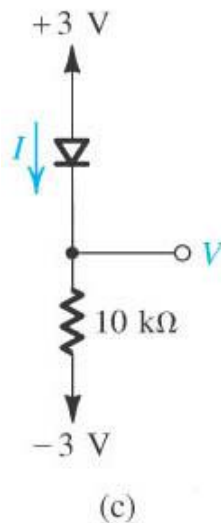

(0.6mA, 3V)

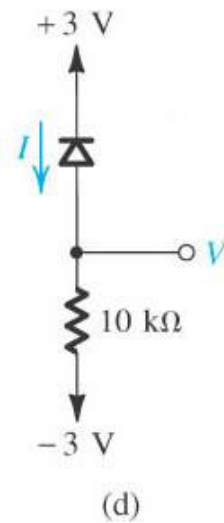

(0mA, -3V)

Problem 2:

1. A small discrete silicon diode is found to conduct $100\ \mu\text{A}$ at 0.7 V and 1mA at 0.815 V. Find the values of I_S and η which correspond.

(Ans. $I_S=8.32 \times 10^{-11}\text{A}$, $\eta \approx 2$)

2. A diode for which $\eta=1$ conducts 0.1mA at 0.7 V. Find its voltage drop at 1mA. For what current is its voltage drop equal 0.815V?

(Ans. 0.758V, 9.95mA)

Problem 3:

A diode described by the exponential characteristic and the battery & resistor model of Fig.1 is connected to a source as shown in Fig.2. Draw the load line and find operating points (I_D and V_D) for:

- (a) $V_{DD} = 1V$, $R = 100\Omega$
- (b) $V_{DD} = 0.9V$, $R = 100\Omega$
- (c) $V_{DD} = 0.9V$, $R = 90\Omega$

(Ans:(a) $V_D = 0.75V$, $I_D = 2.5mA$, (b) $V_D = 0.73V$, $I_D = 1.7mA$, (c) $V_D = 0.74V$, $I_D = 1.8mA$)

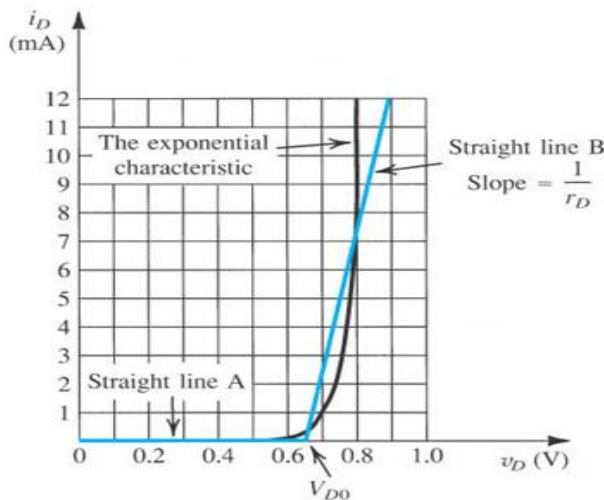


Fig.1

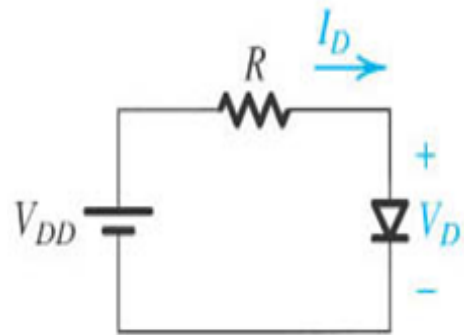


Fig.2

Problem 4:

For the circuit shown in Fig.3, find the current 'I'? [$V_{Threshold} = 0.6V$]

(Ans: $I = 0.9mA$)

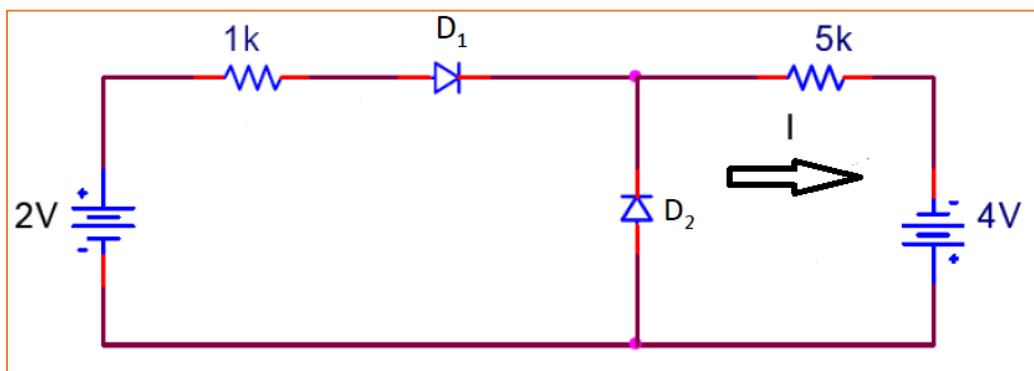


Fig.3

Problem 5:

For the passive symmetric hard limiter shown in Fig.4:

- Find the upper and lower limiting levels (including a 0.7 V diode drop), the gain, and the upper and lower input thresholds levels.
- What is the input current required at twice the upper threshold value?
- Sketch the output voltage versus time at sinusoidal signal input voltage of amplitude 15V and frequency 1KHz

(Ans.: 3V, -3V, 0.5, 6V, -6V, 0.9mA)

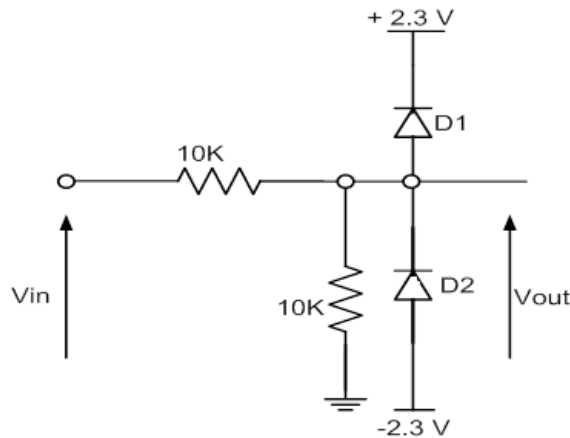


Fig.4

Problem 6:

Sketch the I-V Input characteristic of the circuit of Fig.5 When:

- The switch is open
- The switch is closed

(Assuming the Diode is ideal)


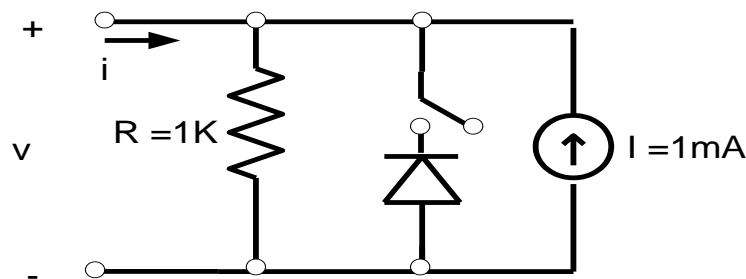
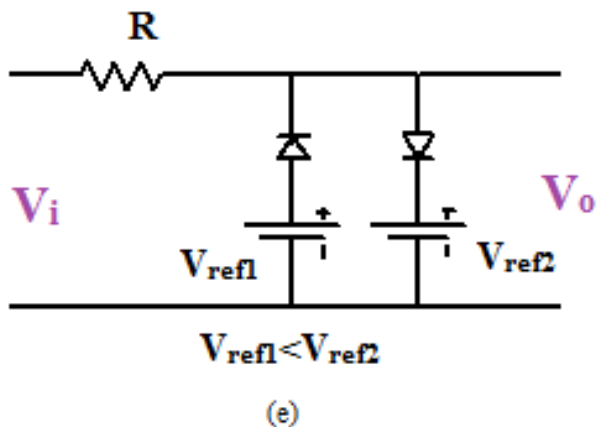
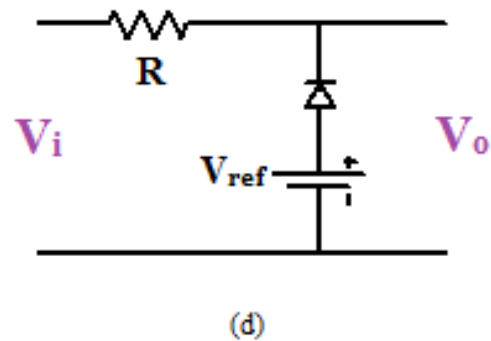
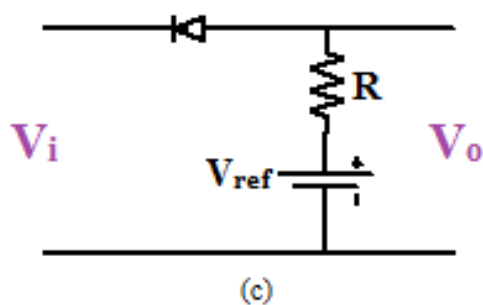
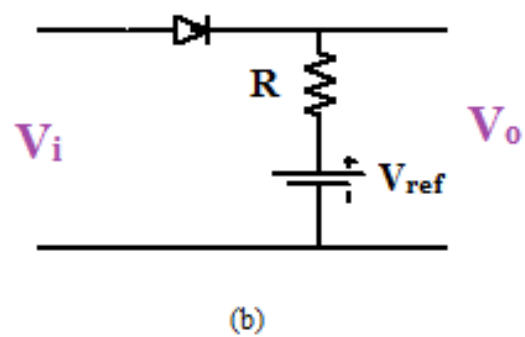


Fig.5


Problem 7:

For the following circuits, assume the diodes are ideal diodes, find ' V_o '? Draw ' V_o ' versus ' V_i '

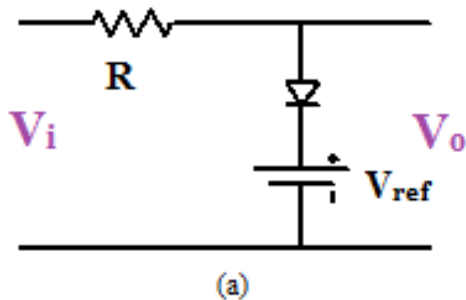

Problem 8:

Sketch the waveform resulting at ' V_o ' for ' V_i ' is a 1-kHz 10-V peak sine wave (assuming ideal diode approximation)

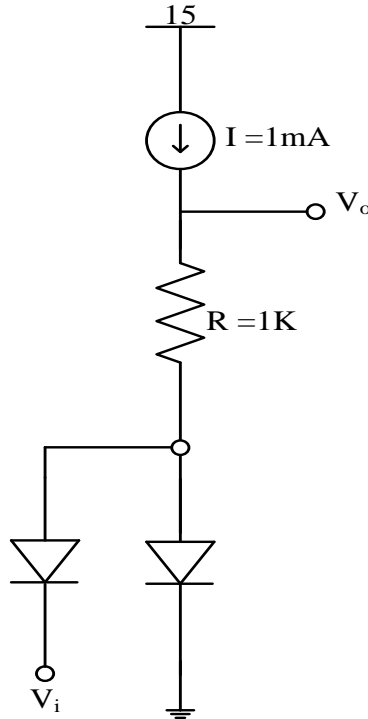

Problem 9:

The circuit shown is a model for a battery charger, ' V_i ' is a 10-V peak sine wave, D_1 and D_2 are ideal diodes, I is a 100-mA current Source and B is a 4.5-V battery. Sketch the waveform of the battery current.

