

## \*BJT AC analysis\*

→ for any Input → obtain DC analysis to get  $I_c$  & make sure BJT is working as an Amplifier (in Active Region)


→ obtain AC analysis to get  $R_{in}$ ,  $R_{out}$ ,  $A_v$

### \* Solution Steps :

① obtain DC analysis to get  $I_c$   $\left\{ \begin{array}{l} \text{Cap} \rightarrow \text{O.C} \\ \text{AC Voltage Source} \rightarrow \text{S.C} \\ \text{AC Current Source} \rightarrow \text{O.C} \end{array} \right.$

②  $g$  from  $I_c$   $\rightarrow g_m = \frac{I_c}{V_T}$   
 $\rightarrow r_{\pi} = \beta / g_m$   
 $\rightarrow r_o = \frac{V_A}{I_c} \rightarrow \text{Early Voltage}$

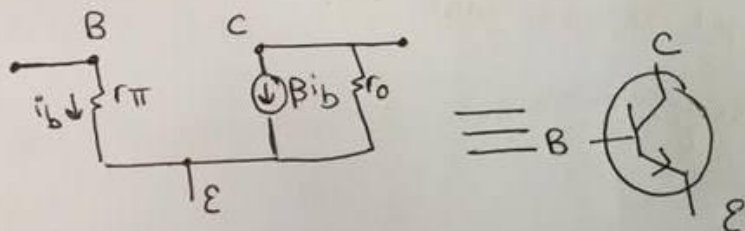③ AC analysis : Remove the transistor & put the small signal model instead.



in AC analysis  $\rightarrow$  Cap  $\rightarrow$  S.C  
DC V.S  $\rightarrow$  S.C  
DC C.S  $\rightarrow$  O.C

⑤  $A_v (\text{gain}) = \frac{V_o}{V_i}$

$$R_{out} = \frac{V_T}{I_T} \Big|_{V_{in} = 0}$$

$$R_{in} = \frac{V_{in}}{I_{in}}$$

\* Important notes :-

1] If  $V_A$  is not given  $\rightarrow$  Assume  $r_o = \infty$

2] For getting  $R_{out}$ , you apply Same Rule as thevenin; where you switch off the independent AC source, Apply  $V_T$  &  $I_T$  @  $V_{out}$  & solve to get  $\boxed{\frac{V_T}{I_T}}$ .

3] check whether  $i_B = 0$  or not for  $R_{out}$  especially, as if it's equal to zero the  $(\beta i_B)$  dependant circuit will become an o.c.

4] Common Emitter means that  $V_{in}$  is on B/C &  $V_o$  is from B/C,  
Common Base means that  $V_{in}$  is on E/C &  $V_o$  is taken from E/C


Same for common collector,  $V_{in} \rightarrow E/B$   
 $V_o \rightarrow E/B$

5] For solving, you can get the gain first then  $R_{in}$  &  $R_{out}$  or vice versa. Both are okay.

①  $R_s = 100 \Omega$ ,  $R_E = 4.3 K$ ,  $R_C = 2.2 K$ ,  $R_3 = 51 K$  &  $\beta = 100$

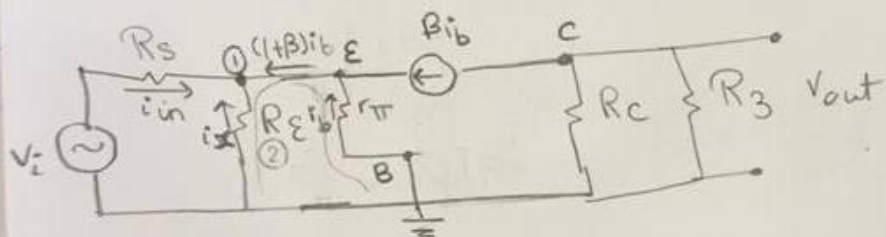a) for  $A_v$ ,  $R_{in}$  &  $R_{out}$  @  $I_C = 1 mA$

→ Draw Small Signal Model :- (cap. SC, DC voltage sources SC)



$$g_m = \frac{I_C}{V_T} = \frac{1 mA}{25 mV} = 40 mA/V$$


$$r_{\pi} = \beta / g_m = 100 / 40 m = 2.5 K\Omega$$

$$r_o = \frac{V_A}{I_C}, \because V_A \text{ not given} \rightarrow r_o \approx \infty$$

→ AC analysis :-

$$V_{out} = -\beta i_b \times R_{out}$$

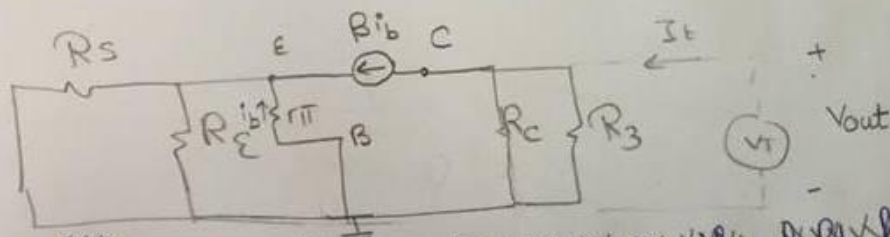→ to get  $R_{out} \rightarrow V_{in} SC$ , add  $V_T$  &  $I_T$



~~→  $V_T$  is off since there is no current in the left half of the circuit.~~  
~~→  $I_T$  is off since there is no current in the right half of the circuit.~~  
 $I_b$  is zero as there's no source conducting  $i_b$  in the left half of the circuit.

$$\therefore \frac{V_T}{I_T} = R_{out} = R_C \parallel R_3 = 2.2 K\Omega \parallel 51 K\Omega$$

$$\boxed{= 2.11 K\Omega}$$



to get  $R_{in}$  :-

(2)

$$\frac{V_{in}}{i_{in}} = R_{in}$$

$i_{in} \rightarrow$  by KCL @ node ① :-

$$i_{in} = -i_x - (1+\beta)i_b \rightarrow \textcircled{1}$$

KVL @ loop ②

$$R_E i_x = -i_b r_{\pi} \rightarrow i_x = \frac{-i_b r_{\pi}}{R_E} \rightarrow \textcircled{2}$$

$\rightarrow$  Substitute in ① :-

$$i_{in} = -\left(1+\beta + \frac{r_{\pi}}{R_E}\right) i_b \rightarrow \textcircled{3}$$

$$\therefore \frac{V_{in}}{i_{in}} = R_S i_{in} + r_{\pi} i_b$$

$$V_{in} = R_S i_{in} + (-R_E i_x)$$

$$= R_S i_{in} - i_b r_{\pi} = R_S i_{in} + \frac{r_{\pi} i_{in}}{\left(1+\beta + \frac{r_{\pi}}{R_E}\right)}$$

$$\frac{V_{in}}{i_{in}} = R_S + \frac{r_{\pi}}{1+\beta + \frac{r_{\pi}}{R_E}} = 124.6 \Omega = R_{in}$$

$$\frac{V_o}{V_{in}} = \frac{\beta i_b \times R_{out}}{R_S \times \left(1+\beta + \frac{r_{\pi}}{R_E}\right) i_b + i_b r_{\pi}}$$

$$\text{gain} \Rightarrow = \frac{\beta \times R_{out}}{R_S \times \left(1+\beta + \frac{r_{\pi}}{R_E}\right) + r_{\pi}}$$

$V_{in}$  in terms of  $i_b$  :-

$$R_S i_{in} - i_b r_{\pi}$$

$$V_{in} = R_S \times \left(-1+\beta + \frac{r_{\pi}}{R_E}\right) i_b - i_b r_{\pi}$$

b)  $I_C = 10 \mu A$ ,  $R_E = 430 K$ ,  $R_C = 220 K$ ,  $R_3 = 510 K$

(3)

→ Same steps as (a)

$$g_m = \frac{I_C}{V_T} = \frac{10 \mu A}{25 mV} = 0.4 mA/V$$

$$r_{\pi} = \beta / g_m = \frac{100}{0.4 m} = 250 K\Omega$$

$$r_o = \infty$$

$$R_{out} = R_C \parallel R_3 = 220 K \parallel 510 K$$
$$= 153.7 K\Omega$$

$$R_{in} = R_S + \frac{r_{\pi}}{1 + \beta + \frac{r_{\pi}}{R_E}} = 2.561 K\Omega$$

$$A_v = \frac{V_{out}}{v_{in}} = \frac{\beta R_{out}}{R_S * (1 + \beta + \frac{r_{\pi}}{R_E}) + r_{\pi}}$$


Problem (2) :-

(4)

$$R_S = 2K, R_1 = 100K, R_2 = 300K, R_3 = 13K, R_4 = 100K, \beta = 100$$

$$I_C = 0.25 \text{ mA}$$

Small signal Model :-

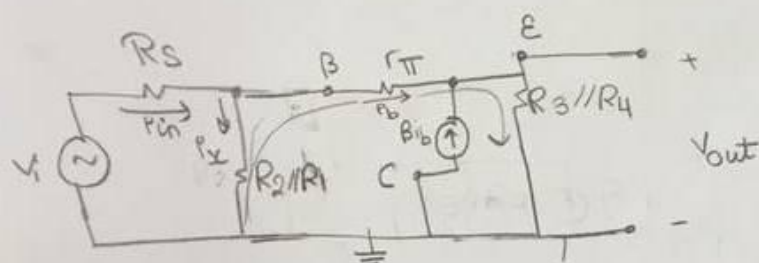

$$g_m = \frac{I_C}{V_T} = \frac{0.25 \text{ mA}}{25 \text{ mV}} = 10 \text{ mA/V}$$

$$r_{\pi} = \beta / g_m = 100 / 10 \text{ m} = 10 \text{ K}$$

$$r_o = \infty$$

→ to get  $R_{in}$  :-

$$V_{in} = i_{in} \times R_{in}$$

$$i_{in} = i_b + i_x$$

KVL @ loop ① :-

$$-i_x (R_2 || R_1) + i_b r_{\pi} + (1 + \beta) i_b \times R_3 || R_4 = 0$$

$$i_x = -i_b \frac{r_{\pi} + (1 + \beta) \times R_3 || R_4}{R_2 || R_1}$$

$$\therefore i_{in} = i_b + i_b \times \frac{r_{\pi} + (1 + \beta) \times R_3 || R_4}{R_2 || R_1} \rightarrow i_b = \frac{i_{in}}{1 + \frac{r_{\pi} + (1 + \beta) \times R_3 || R_4}{R_2 || R_1}}$$

$$R_{in} = \frac{V_{in}}{i_{in}}$$


(5)

$$V_{in} = R_s \times i_{in} + i_b (r_{\pi} + (1+\beta) R_3 // R_4)$$

$$= R_s \times i_{in} + \frac{i_{in}}{1 + \frac{r_{\pi} + (1+\beta) R_3 // R_4}{R_1 // R_2}} \times r_{\pi} + (1+\beta) R_3 // R_4$$

$$\frac{V_{in}}{i_{in}} = R_s + R_1 // R_2 \times \frac{r_{\pi} + (1+\beta) R_3 // R_4}{1 + r_{\pi} + (1+\beta) R_3 // R_4} \Rightarrow R_{in}$$

→ to get  $R_{out}$  :-

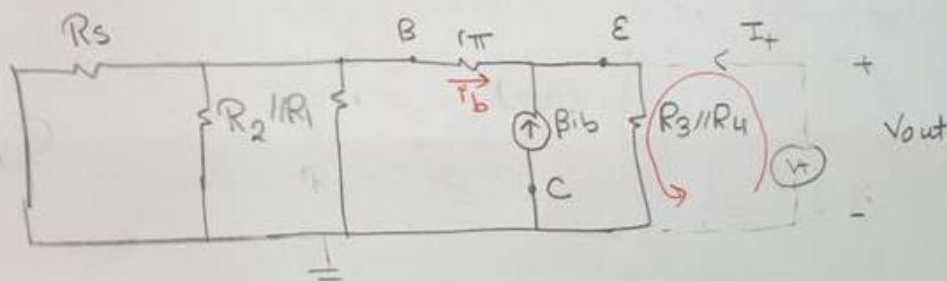

$$V_T = (I_t + \beta i_b + i_b) * R_3 // R_4$$

$$\therefore V_T = V_E \text{ \& } i_b = \frac{-V_T}{(R_s // R_2 // R_1) + r_{\pi}}$$

$$V_t = \left( I_t + \frac{(1+\beta) * -V_T}{(R_s // R_2 // R_1) + r_{\pi}} \right) * R_3 // R_4$$

$$V_t \left( \frac{1}{R_3 // R_4} + \frac{1+\beta}{(R_s // R_2 // R_1) + r_{\pi}} \right) = I_t$$

$$\frac{V_t}{I_t} = \frac{1}{\frac{1}{R_3 // R_4} + \frac{1+\beta}{(R_s // R_2 // R_1) + r_{\pi}}} \rightarrow R_{out}$$




$$V_{out} = (1+\beta)i_b \times (R_3 // R_4)$$

⑥

$$\frac{V_o}{V_i} = \frac{(1+\beta) \times (R_3 // R_4)}{R_s \left(1 + \frac{r_{\pi} + (1+\beta) R_3 // R_4}{R_1 // R_2}\right) + (r_{\pi} + (1+\beta) R_3 // R_4)} \rightarrow \text{gain}$$

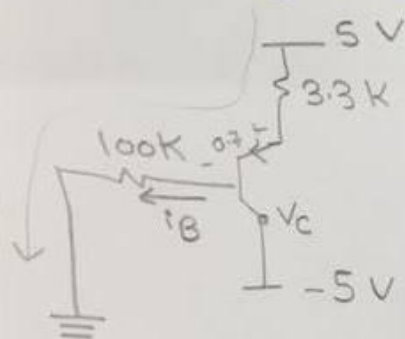Problem ③ ∴

→ First we need to get  $I_c$  as it's not given, thus we have to solve with DC-analysis first.



$$-5 + 3.3K I_E + 0.7 + 100K I_B = 0$$

$$-5 + 3.3K(1+\beta)I_B + 0.7 + 100K I_B = 0$$

$$-4.3 + 499.3K I_B = 0$$

$$I_B = 8.61 \mu A$$


$$I_C = 1.03 \text{ mA}$$

$$V_{CE} > 0.2 \checkmark \text{ Active}$$

→ Second we need to solve using the small signal model.



(7)

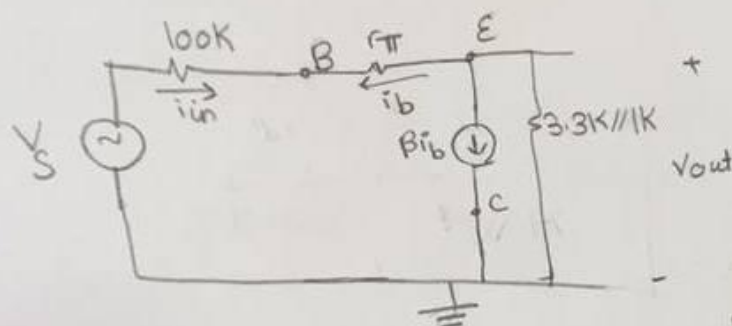

Note: AC Model for PNP is the same as NPN, Just notice the currents direction.

$$g_m = \frac{I_c}{V_T}$$

$$r_{\pi} = \beta / g_m$$

$$r_o = \infty$$

to get  $R_{in}$  :-

$$\frac{V_{in}}{i_{in}} = R_{in}$$

$$\rightarrow V_{in} = 100K \times i_{in} - r_{\pi} i_b - (3.3K // 1K) \times (1+\beta) i_b$$

$$\because i_{in} = -i_b$$


$$\therefore \frac{V_{in}}{i_{in}} = 100K + r_{\pi} + (3.3K // 1K) \times (1+\beta) \Rightarrow R_{in}$$

$$V_{in} = i_{in} \times R_{in}$$

$$V_{out} = (1+\beta) i_b \times (3.3K // 1K)$$

for Rout

8

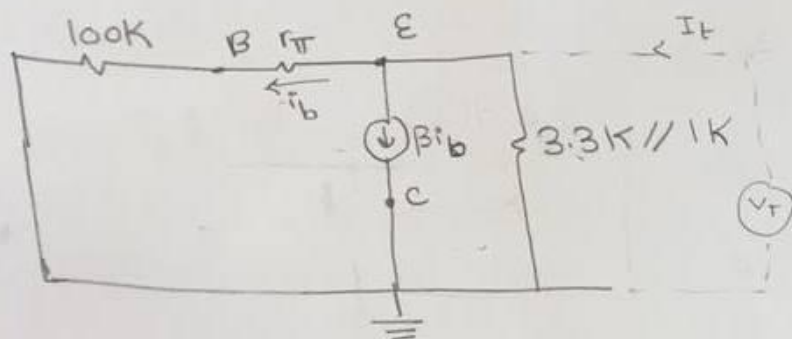

$$V_T = 1K // 3.3K * (I_t - \beta i_b - i_b)$$

$$\therefore V_T = V_E \text{ \& } i_b = \frac{V_T}{R_{\pi} + 100K}$$

$$V_T = 1K // 3.3K * \left( I_t - \frac{\beta V_T}{R_{\pi} + 100K} - \frac{V_T}{R_{\pi} + 100K} \right)$$

$$\frac{V_T}{1K // 3.3K} + \frac{(1+\beta) V_T}{R_{\pi} + 100K} = I_t$$

$$V_T \left( \frac{1}{1K // 3.3K} + \frac{1+\beta}{R_{\pi} + 100K} \right) = I_t$$


$$\frac{V_T}{I_t} = \frac{1}{\frac{1}{1K // 3.3K} + \frac{1+\beta}{R_{\pi} + 100K}} \rightarrow R_{out}$$

$$\frac{V_o}{v_i} = \frac{(1+\beta) * (3.3K // 1K)}{100K + R_{\pi} + [(1+\beta) * (3.3K // 1K)]} \rightarrow \text{gain}$$

# Problem (4)

9

DC-analysis :-

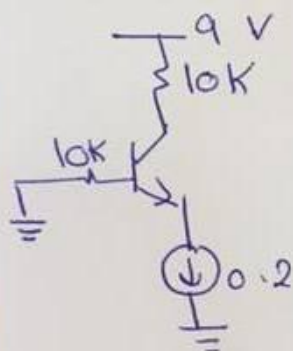

$$I_E = 0.2 \text{ mA}$$

$$(1 + \beta) I_B = 0.2 \text{ mA}$$

$$I_B = 3.92 \text{ } \mu\text{A}$$

$$I_C = 0.196 \text{ mA}$$


$$V_{CE} > 0.2 \checkmark \rightarrow \text{Active}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.196 \text{ mA}}{25 \text{ mV}} = 7.84 \text{ mA/V}$$

$$r_\pi = \beta / g_m = \frac{50}{7.84 \text{ m}} = 6.38 \text{ k}\Omega$$

$$r_o = \infty$$

→ AC-analysis :-

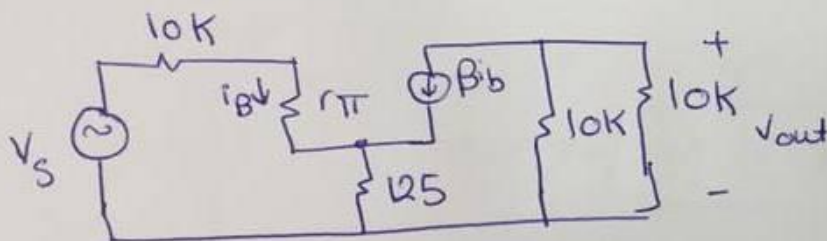

$$V_{out} = -\beta i_b \times R_{out}$$

$$V_{in} = i_b \times R_{in}$$

$$\frac{V_o}{V_i} = \frac{-\beta R_{out}}{R_{in}} \rightarrow \text{gain}$$




(10)

$$V_s = 10K i_b + r_{\pi} i_b + (1+\beta) i_b \times 125$$

$$\therefore i_b = i_{in}$$

$$\frac{V_s}{i_b} = 10K + r_{\pi} + (1+\beta) \times 125 \rightarrow R_{in}$$

for  $R_{out}$

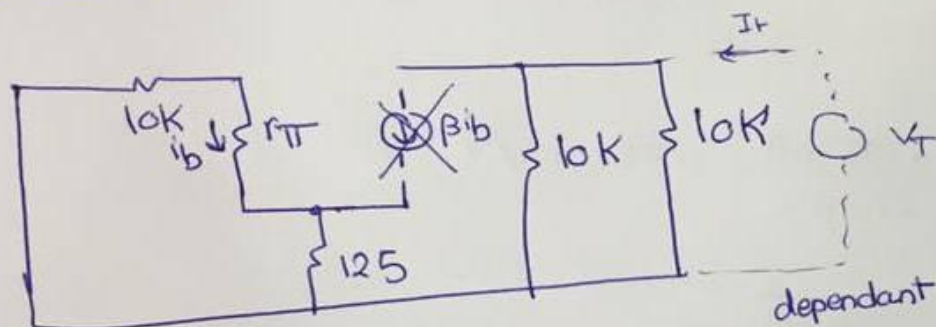

→ To check whether  $i_b = 0$  or not, we close the current source & check whether there's any source driving the current needed ( $I_b$ ). In this case,  $I_b = 0$  as there's no source to produce the current, thus  $\beta I_b$  is an o.c.


$$\therefore \frac{V_T}{I_T} = 10K // 10K = 5K \rightarrow R_{out}$$

$$\frac{V_o}{V_i} = \frac{-\beta \times 5K}{10K + r_{\pi} + (1+\beta) \times 125} \rightarrow \text{gain}$$

# \*problem 5

11

## -DC analysis:-

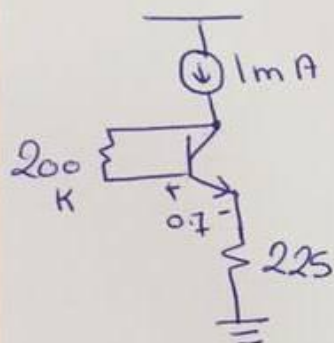

$$I_C + I_B = 1 \text{ mA}$$

$$\beta I_B + I_B = 1 \text{ mA}$$

$$I_B = 9.9 \mu\text{A}$$

$$I_C = 0.99 \text{ mA}$$


check for  $V_{CE} > 0.2 \checkmark$

$$g_m = \frac{0.99 \text{ mA}}{25 \text{ mV}} = 0.0396 \text{ mA/V}$$

$$r_\pi = \beta / g_m = 2.5 \text{ K}\Omega$$

$$r_o = \infty$$

## AC-analysis :-

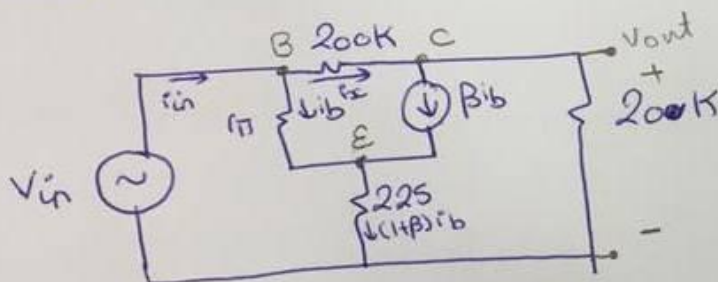

To get  $R_{in}$  :-

$$V_{in} = i_b (r_\pi + (1+\beta) \times 225) \rightarrow (1)$$

$$V_{in} = 200K i_x + (i_x - \beta i_b) \times 20K \rightarrow (2)$$

$$V_{in} = 200K (i_{in} - i_b) + (i_{in} - \beta i_b) \times 20K$$

$$V_{in} = i_{in} (200K + 20K) - i_b (200K + (1+\beta) 20K)$$

(12)


$$V_{in} = i_n(20k + 200k) - V_{in} \frac{(225 + (\beta+1)20k)}{r_{\pi} + (\beta+1) \times 225}$$

$$V_{in} \left[ 1 + \frac{225 + 20k(1+\beta)}{r_{\pi} + (1+\beta) \times 225} \right] = i_n (20k + 200k)$$

$$\boxed{\frac{V_{in}}{I_{in}} = \frac{20k + 200k}{1 + \frac{225 + 20k(1+\beta)}{r_{\pi} + (1+\beta) \times 225}}} \rightarrow R_{in}$$



(13)

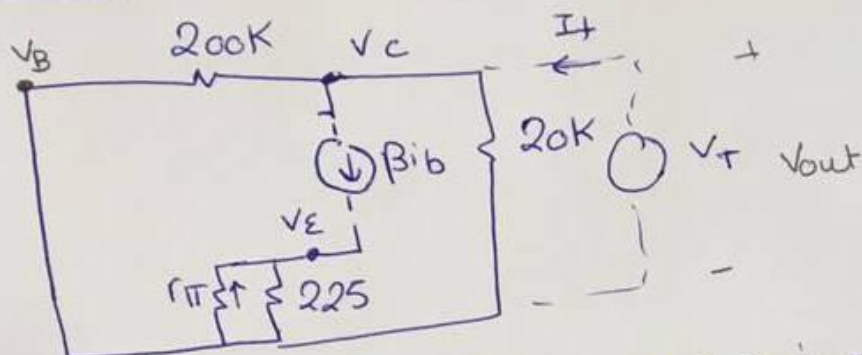→ to get  $R_{out}$  ∴

→ Same case as problem (4),  $\beta i_b$  is an O.C as  $i_b = 0$ .

$$\therefore \frac{V_T}{I_T} = R_{out} = 20k \parallel 200k$$

$$= 18.18k$$

~~to~~ to get gain ∴

$$\frac{V_o}{20k} + \beta i_b + \frac{V_o - V_i}{200k} = 0$$

$$V_o \left( \frac{1}{20k} + \frac{1}{200k} \right) = \frac{V_i}{200k} + \frac{-\beta V_i}{r_{\pi} + (1+\beta) \times 225}$$

$$\frac{V_o}{V_i} = \frac{\frac{1}{20k} + \frac{-\beta}{r_{\pi} + (1+\beta) \times 225}}{\frac{1}{20k} + \frac{1}{200k}}$$

$$= \frac{200k \parallel [(r_{\pi} + (1+\beta) \times 225) \times -\beta]}{20k \parallel 200k} \rightarrow \text{gain}$$

Best of Luck 😊