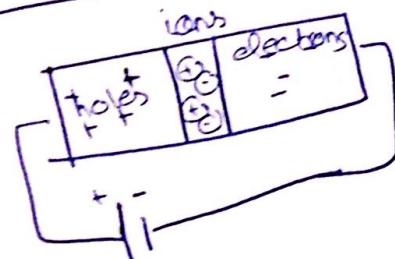


①

Diodes


① P-N junction :-




- Forward & Reverse Biased
- Diffusion & drift currents

Anode \downarrow cathode

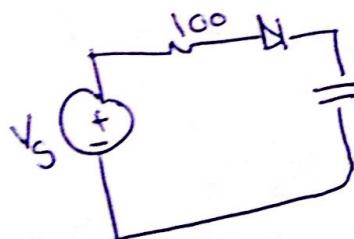- ideal Diode is Represented as a SC if On & OC if off.
- The diodes can be used as Rectifiers or logic gates ...



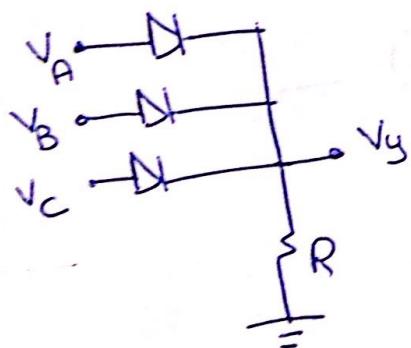
$12V \rightarrow$ Rectifier \rightarrow operates only in the +ve half cycle of the V_s .



$\text{OR gate} \rightarrow$ if any of the diodes are on, V_y will have a value

*what if we don't know which diode is conducting? We make a plausible assumption, proceed with the analysis & then check whether we end up with a consistent solution.

→ IV characteristics

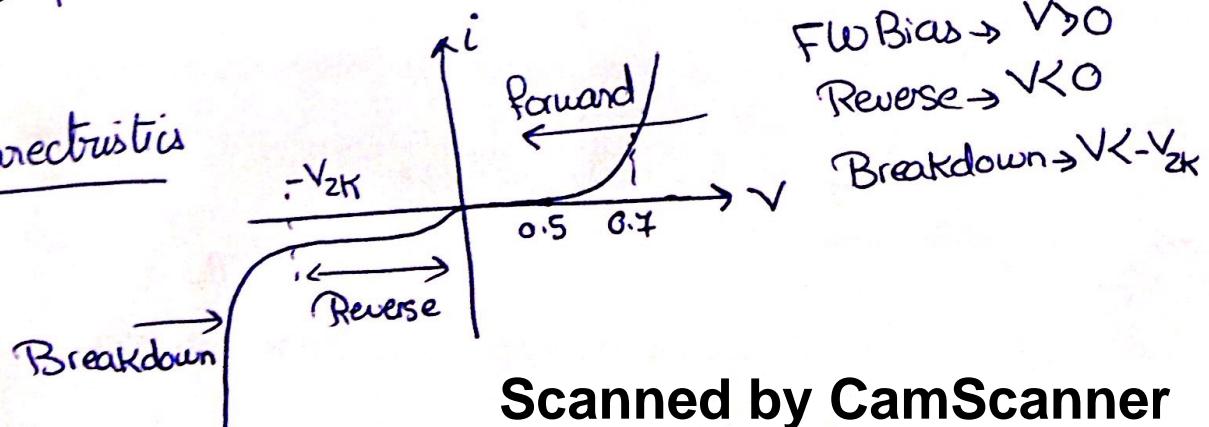

*forward Bias Region:-

$$i = I_s (e^{V_{NT}} - 1) \approx I_s e^{V_{NT}}$$

η : ideally = 1 (depends on material)

(2)

I_s : Saturation current \propto Diode cross sectional Area.

Boltzmann's constant

V_T : thermal voltage : $V_T = \frac{RT}{q}$

R → absolute Temp. in Kelvin

q → Magnitude of Electronic charge

$$\rightarrow \frac{I_2}{I_1} = e^{\frac{(V_2 - V_1)}{V_T}}$$

* Reverse-Bias Region:-


$$i \approx I_s$$

* Breakdown Region:-

→ It's Entered when the magnitude of the Reverse Voltage exceeds a threshold value called the Breakdown Voltage

* Diode Models:-

ideal :-

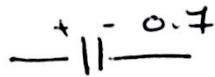


*Sheet 2 Solution *


①

Problem 1 :-

a) Find I & V

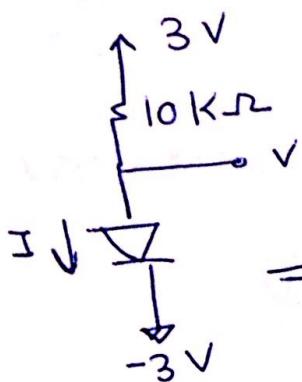


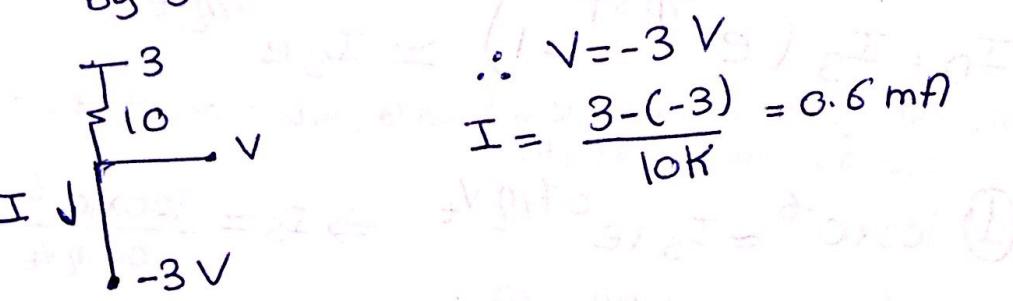→ the diode is on & FW biased → Replaced by short circuit




$$\therefore V = -3 \text{ V}$$
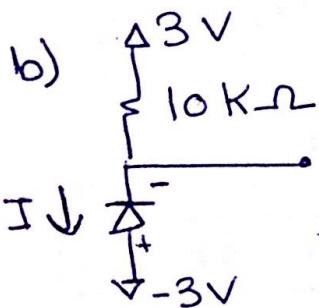
$$I = \frac{3 - (-3)}{10 \text{ k}} = 0.6 \text{ mA}$$




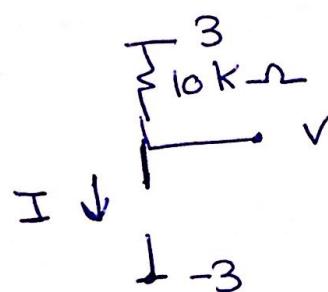→ the diodes is off → Replaced by open circuit



$$\therefore V = 3 \text{ V}$$


$$I = \text{zero.}$$

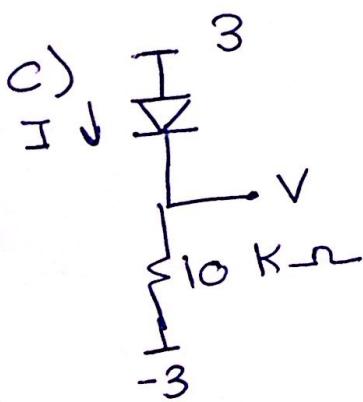


→ the diode is on → Replaced by SC

$$V = 3 \text{ V}$$
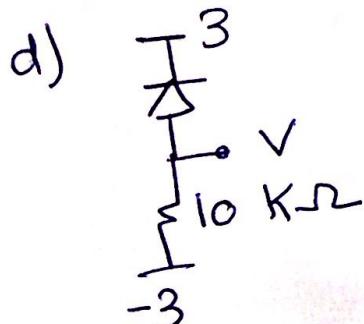
$$I = \frac{3 - (-3)}{10 \text{ k}} = 0.6 \text{ mA}$$



→ the diode is off → Replaced by OC

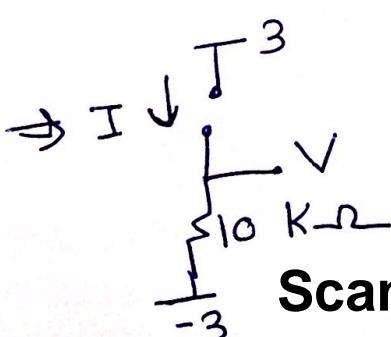

$$V = -3 \text{ V}$$

$$I = \text{zero.}$$

(2)

Problem 2 :

$$I_D = 100 \text{ } \mu\text{A} @ V = 0.7 \text{ V}$$

$$I_D = 1 \text{ mA} @ 0.815 \text{ V}$$

$$I_D = I_S (e^{\frac{V}{2} - 1}) \approx I_S e^{\frac{V}{2}}$$

A small discrete Silicon diode is found to conduct 100 μA at 0.7 V & 1 mA at 0.815 V
Find the values of I_S & V_t .

$$\textcircled{1} \quad 100 \times 10^{-6} = I_S e^{0.7/2} \Rightarrow I_S = \frac{100 \times 10^{-6}}{e^{0.7/2}} \quad \textcircled{1}$$

$$1 \times 10^{-3} = I_S e^{0.815/2} \quad \textcircled{2}$$

$$\therefore 1 \times 10^{-3} = \frac{100 \times 10^{-6}}{e^{0.7/2}} e^{0.815/2}$$

$$1 \times 10^{-3} = 100 \times 10^{-6} e^{\frac{1}{2} (0.115)}$$

$$\ln\left(\frac{1 \times 10^{-3}}{100 \times 10^{-6}}\right) = \frac{1}{2} \times 0.115$$

$$\frac{1}{2} = 20.022$$

$$\therefore 2 = 0.0499$$

$$\therefore V_t = 25 \text{ mV} @ 300 \text{ K}$$

$$\boxed{\therefore 2 = 2}$$

By substituting in Either ① or ② :-

$$I_S = 8.085 \times 10^{-11}$$

② A diode for which $\eta=1$ conducts 0.1 mA at 0.7 V. Find the voltage drop at 1 mA. For what current is the voltage drop equal 0.815 V? ③

$$\eta=1 \quad I=0.1 \text{ mA} \quad V=0.7$$

$$V=? @ 1 \text{ mA}$$

$$I_D = I_S e^{\frac{V}{\eta} V_T}$$
$$\rightarrow 0.1 \times 10^{-3} = I_S e^{0.7 / (25 \times 10^{-3})}$$

$$\therefore I_S = 6.9 \times 10^{-17}$$

$$\therefore V = V_T \ln \frac{I}{I_S}$$
$$= 25 \times 10^{-3} \ln \left(\frac{1 \times 10^{-3}}{6.9 \times 10^{-17}} \right)$$
$$= 0.758 \text{ V}$$

$$I_D = 6.9 \times 10^{-17} \times e^{0.815 / (25 \times 10^{-3})}$$
$$= 9.93 \text{ mA}$$

Problem 3 :

→ For the following Example we have to get the intersection between a line we draw & the Exponential characteristic curve.

→ the coordinates of the line are (V, I)

1st point $\rightarrow (0, I)$


2nd point $\rightarrow (V, 0)$

→ get I & V and draw a straight line, then get the intersection with the Exponential charac. curve.

(load line)

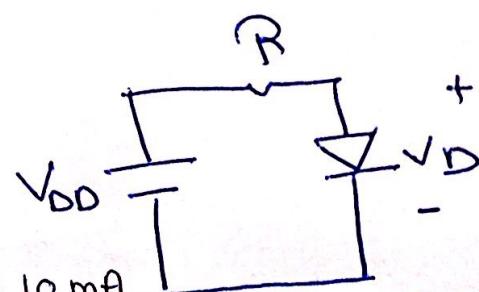a) $V_{DD} = 1 \text{ V}$ $R = 100 \Omega$

→ when $V_D = 0$ (e.g. S.C), $I = \frac{V_{DD}}{R}$
 $= \frac{1 \text{ V}}{100 \Omega} = 10 \text{ mA}$



→ when $I = 0$ (e.g. O.C), $V = V_{DD} \rightarrow V = 1 \text{ V}$

Sol: $V_D = 0.75 \text{ V}$, $I_D = 2.5 \text{ mA}$

b) $V_{DD} = 0.9 \text{ V}$, $R = 100 \Omega$

→ when $V = 0 \rightarrow I = \frac{V_{DD}}{R} = 9 \text{ mA}$

when $I = 0 \rightarrow V = V_{DD} = 0.9 \text{ V}$


Sol: $V_D = 0.73 \text{ V}$, $I = 1.7 \text{ mA}$

c) $V_{DD} = 0.9 \text{ V}$, $R = 90 \Omega$

→ when $V = 0 \rightarrow I = \frac{V_{DD}}{R} = 10 \text{ mA}$


when $I = 0 \rightarrow V = V_{DD} = 0.9 \text{ V}$

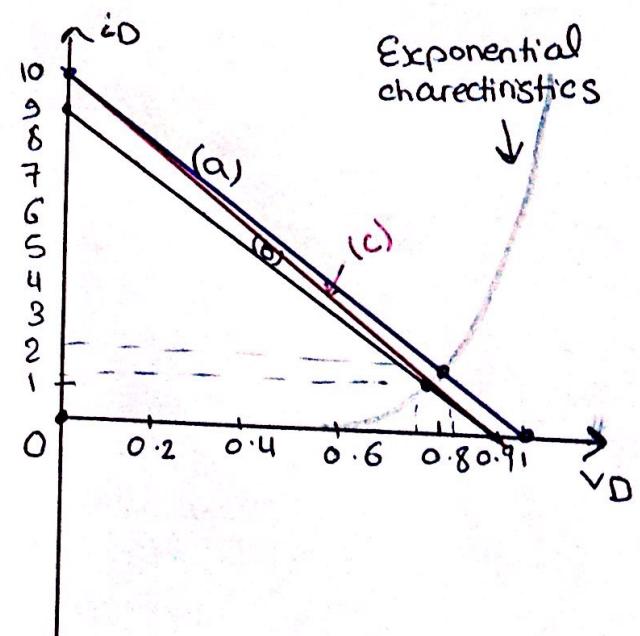Sol: $V_D = 0.74 \text{ V}$, $I_D = 1.8 \text{ mA}$




Problem (4) :

(2)

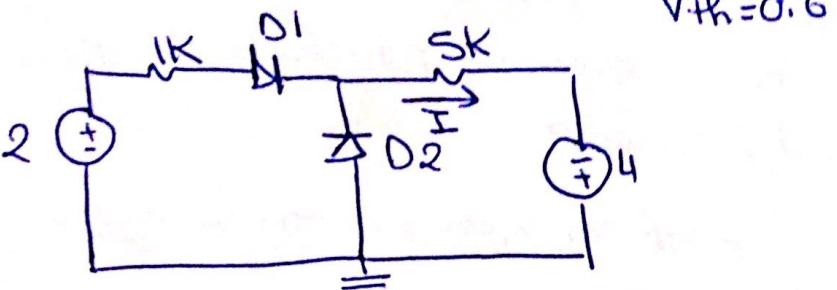

Assume D1 ON & D2 OFF :

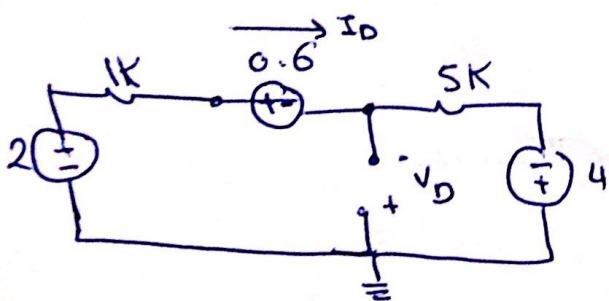

$$-2 + 1KID + 0.6 + 5KID - 4 = 0$$

$$-5.4 + 6KID = 0$$

$$ID = \frac{-5.4}{-6K} \rightarrow +ve \checkmark = 0.9mA$$

check for V_D :

$$V_{O+} = \text{zero}$$

$$V_{O-} = 5KID - 4$$


$$\begin{aligned} &= (0.9)5 - 4 \\ &= 0.5 \end{aligned}$$

$\therefore V_{O-} > V_{O+} \rightarrow D2 \text{ off} \checkmark$

$$\boxed{\therefore I = 0.9mA}$$

wrong Assumption :

D1 off & D2 on :

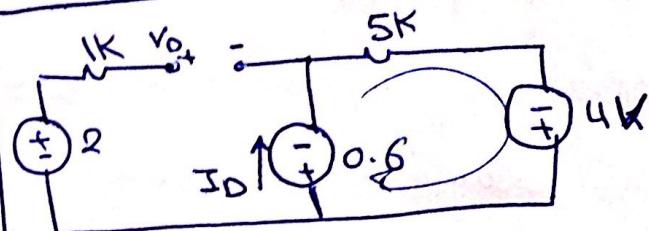

$$0.6 + 5KID - 4K = 0$$

$$-3.4 = -5KID$$

$$ID = 1.6mA \checkmark$$

check for V_D :


$$V_{O+} = 2$$

$$V_{O-} = -0.6$$

\rightarrow the Diode should be on

\therefore Wrong Assumption

Problem 5 :-

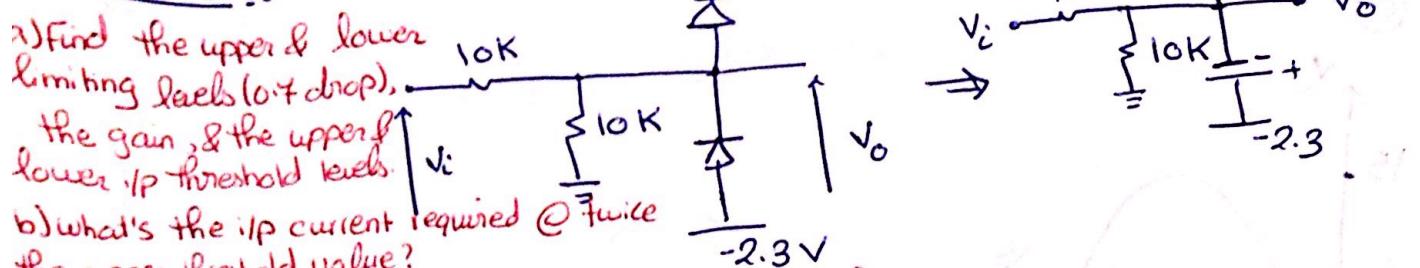

b) what's the i/p current required @ twice the upper threshold value?

c) Sketch V_o vs time @ Sin V_i of amplitude 15V & freq. 1KHz
diodes = 0.7 \rightarrow DC Source = 0.7

• Voltage drops

a) * limiting level? \rightarrow What's the Max Value that V_o can reach?

$$D_1 \text{ ON} \rightarrow V_o > 3V \rightarrow (2.3 + 0.7)$$

$$D_2 \text{ ON} \rightarrow V_o \leq -3V \rightarrow (-2.3 + (-0.7))$$


N.B. V_o will never pass 3 or -3V because the voltage becomes constant as it's taken from 2 DC Sources rather than V_i .

upper & lower input threshold?

\rightarrow At which value will V_o stand depending on the DC Sources instead of V_i ?

1st let's get the circuit gain to know the relation between V_i & V_o .

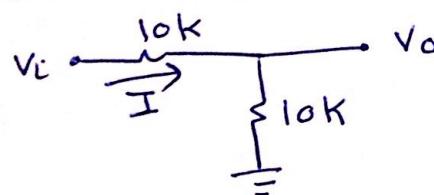\Rightarrow Gain V_o/V_i is when all other DC Sources are off.



$$\frac{V_o}{V_i} = \frac{10k}{10k+10k} = 0.5$$

$$\therefore \text{threshold} \rightarrow \frac{3-3}{V_i} = 0.5 \rightarrow V_i = 6/-6V$$


b) $V_i = 2(\text{upper threshold}) = 12V$

$D_1 \text{ ON} \rightarrow V_o = 3V$ (no increase in V_o if $V_i > 6V$)

$$\Rightarrow \text{i/p current (I in the 1st 10k)} \rightarrow \frac{V_i - V_o}{10k} = \frac{12-3}{10k} = 0.9 \text{ mA}$$

B


F C

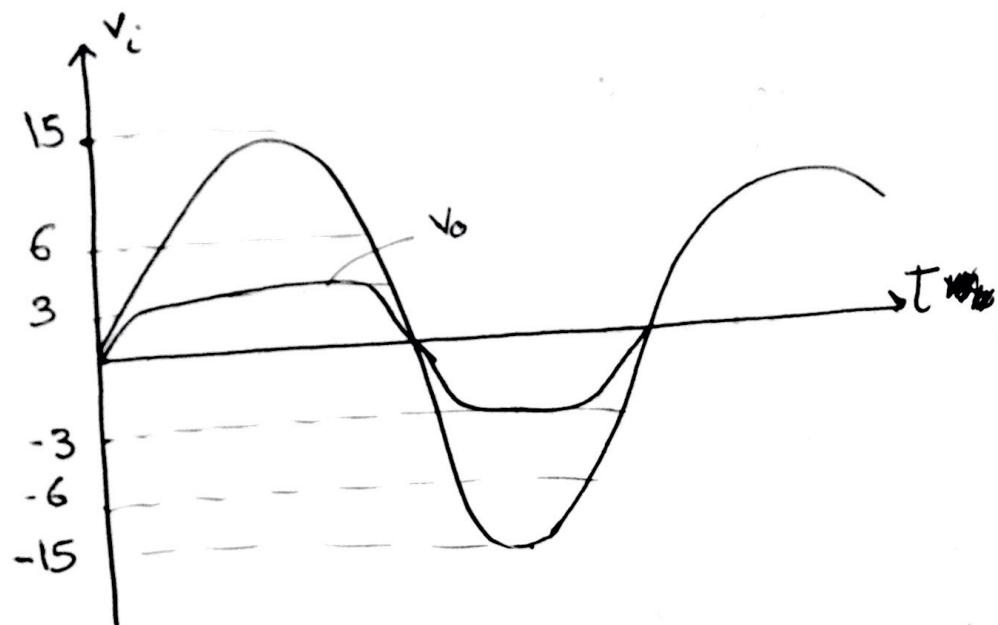




- * When $V_i = 6 \text{ V} \rightarrow \text{Di ON}$, V_o will be sketched to 3V ($2.3 + 0.7$)
- * When $V_i < 6 \text{ V} \rightarrow V_o = 0.5 V_i$
- * Same thing for the negative part.

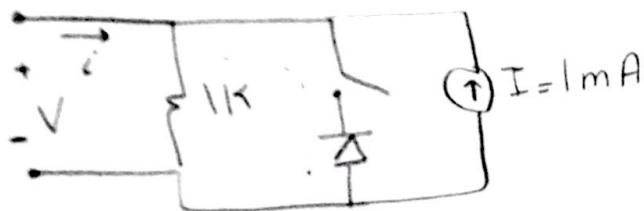Problem 6 :-

Sketch I-V input characteristics of the circuit:



a) when Switch is open:-

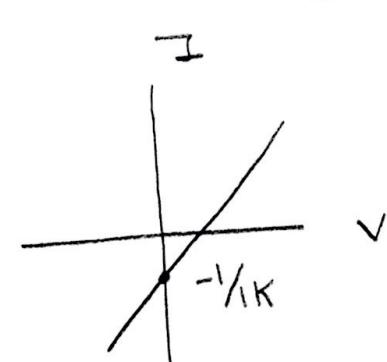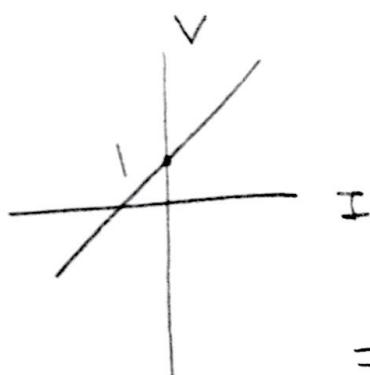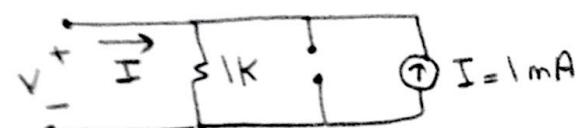

$V = (1\text{mA} + i) \times 1\text{K}$
 \therefore linear relationship between I & V

$$V = (1\text{mA} \times 1\text{K}) + 1\text{K}i$$

$$y = c + mx$$

$$i = \frac{V-1}{1\text{K}} = \frac{V}{1\text{K}} - \frac{1}{1\text{K}} \Rightarrow c$$


b) when Switch is closed :-

if $V < 0 \rightarrow$ Diode becomes short circuit
 $\& I = \infty$




if $V > 0 \rightarrow$ Same linear Relationship as Before

N.B: for any -ve value for V_i , same slope for $\frac{I}{V_i}$.

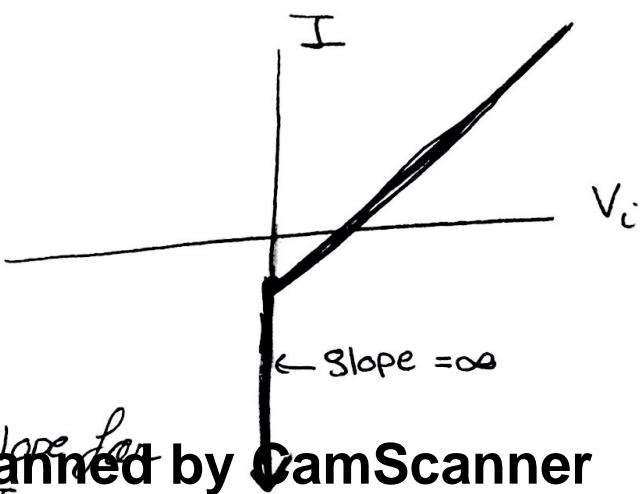



Problem 7

Find V_o , Draw V_o vs V_i .

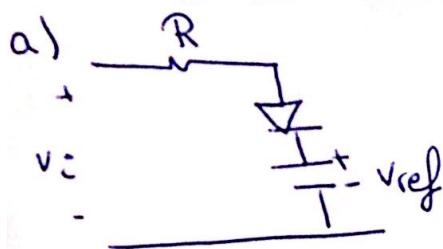



$$\text{if } V_i > V_{\text{ref}} \rightarrow V_o = V_{\text{ref}}$$
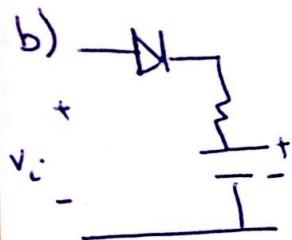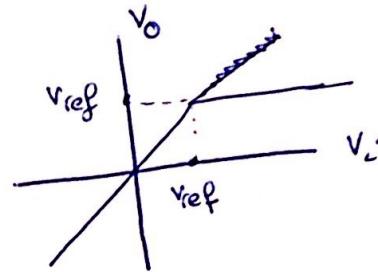
$$V_i < V_{\text{ref}} \rightarrow V_o = V_i$$





$$\text{if } V_i > V_{\text{ref}} \rightarrow V_o = V_i$$
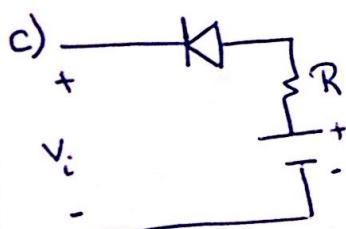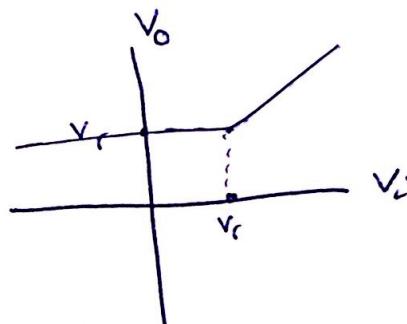
$$V_i < V_{\text{ref}} \rightarrow V_o = V_{\text{ref}}$$





$$\text{if } V_i > V_{\text{ref}} \rightarrow V_o = V_{\text{ref}}$$
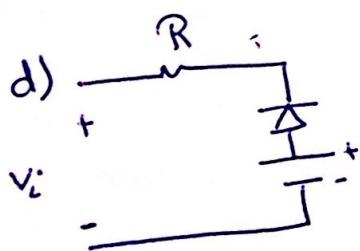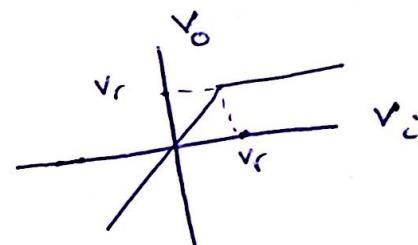
$$V_i < V_{\text{ref}} \rightarrow V_o = V_i$$



$$\text{if } V_i > V_{\text{ref}} \rightarrow V_o = V_i$$

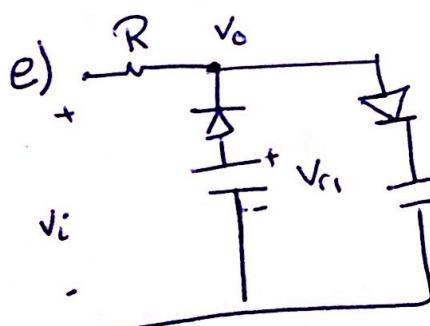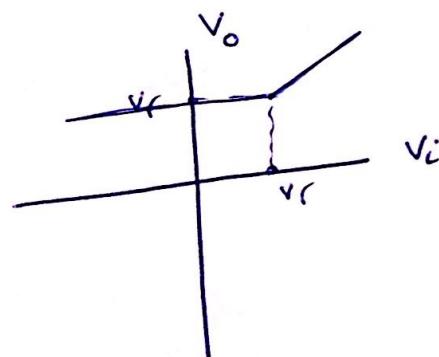
$$V_i < V_{\text{ref}} \rightarrow V_o = V_{\text{ref}}$$



$$\text{if } V_i > V_{r2} \rightarrow V_o = V_{r2}$$

$$\text{if } V_i < V_{r1} \rightarrow V_o = V_{r1}$$
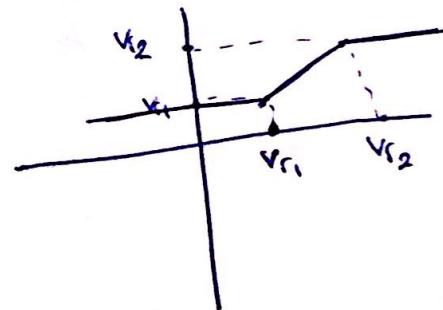
$$\text{if } V_{r1} < V_i < V_{r2} \rightarrow V_o = V_i$$




(8)

problem 8 :-

Sketch V_o for V_i 1K-Hz, 10V Peak Sin wave

$$V_o = 1\text{mA} \times 1\text{K} = 1\text{V} (\text{when +ve})$$

* V_{in} is a Sin wave :-

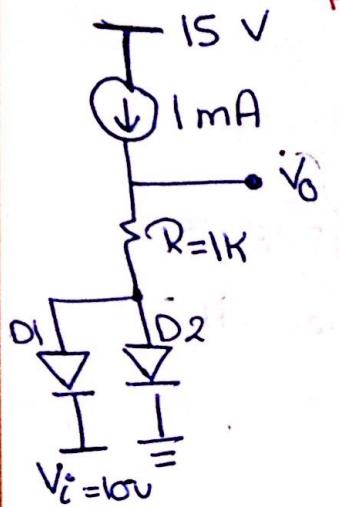


- when +ve D_1 is off $\rightarrow V_i > 0$

D_2 is on

$$V_o = 1\text{V}$$

- when -ve D_1 ON, D_2 OFF $\rightarrow V_i < 0$
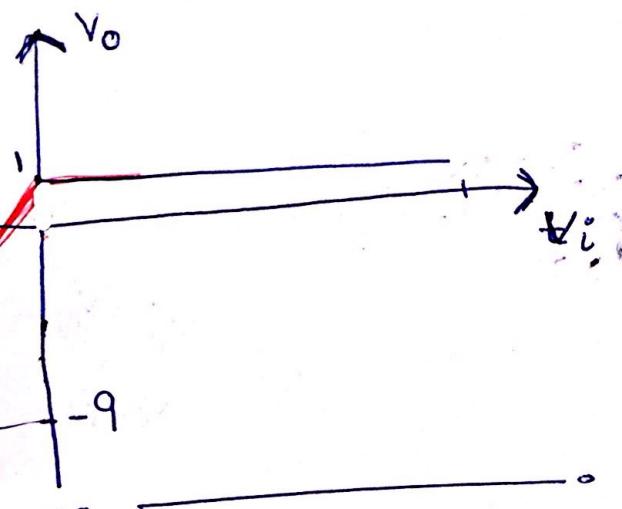
$$\begin{aligned} V_o &= -10 + (1\text{mA} \times 1\text{K} \cdot R) \\ &= -9\text{V} \end{aligned}$$



V_i is a 10-V peak Sine wave
Sketch the waveform of the battery current.


problem 9 :-

Determine i_B Battery :-

$V_i = 10\text{-V peak Sine wave}$

$$I = 100\text{ mA}$$

$$V_B = 4.5\text{ V}$$

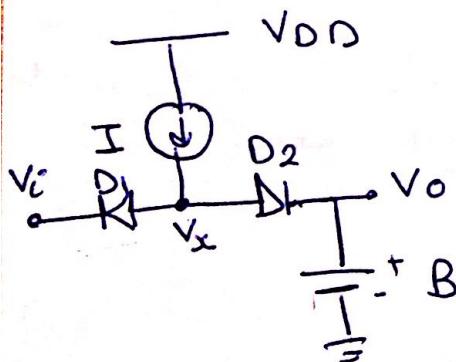

Assuming D_1 ON & D_2 OFF :-

$$\therefore V_x = V_i$$

this can happen only if $V_x < 4.5\text{V}$

@ this case, $i_B = 0$


Assuming D_1 OFF & D_2 ON :-

$$V_x > 4.5 \quad \& \quad V_i > V_x \rightarrow V_i > 4.5$$

$\therefore I = 100\text{ mA}$

Scanned by CamScanner

9

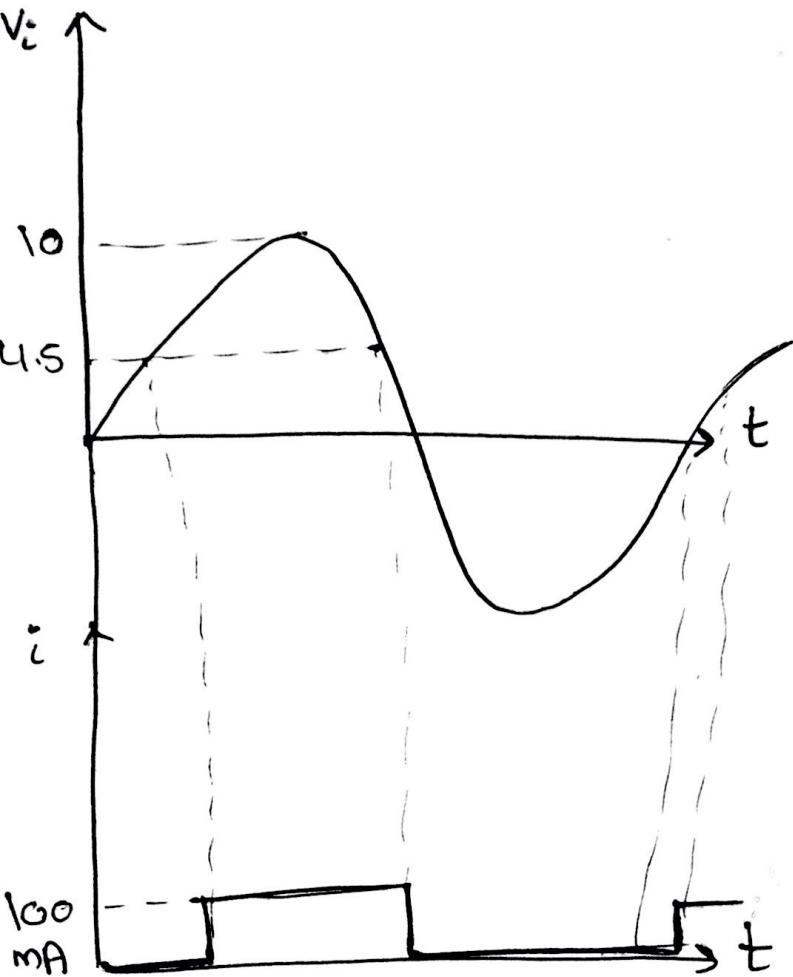

$$V_i < 4.5 \rightarrow i_B = \text{zero}$$

$$V_i > 4.5 \rightarrow i_B = 100 \text{ mA}$$