
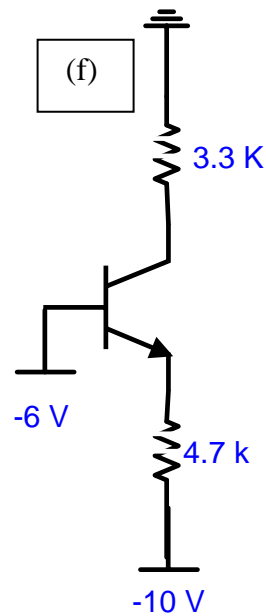
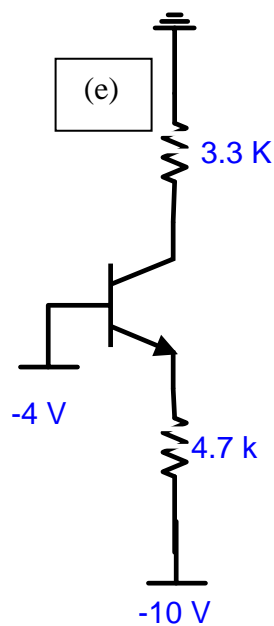
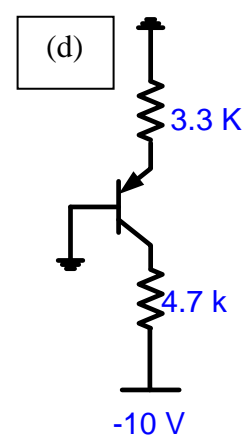
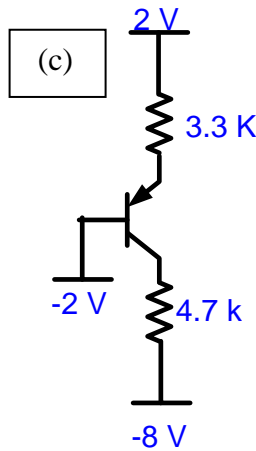
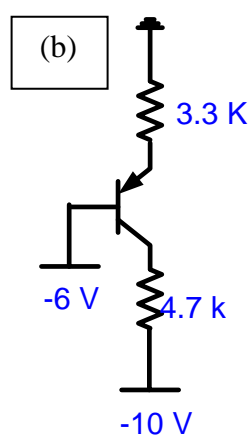


## Sheet 4: BJT DC Analysis

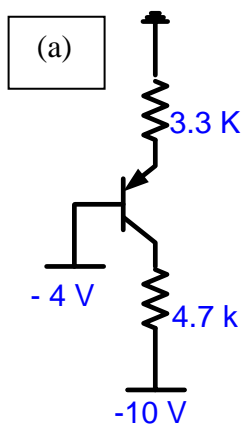
### Problem 1:

For the following circuits, find node voltages,  $V_E$ ,  $V_C$ , and branch currents  $I_E$ ,  $I_C$ ,  $I_B$ . Use  $V_{BE}$  ( or  $V_{EB}$  for PNP transistor) = 0.7 V and  $\beta=50$ .


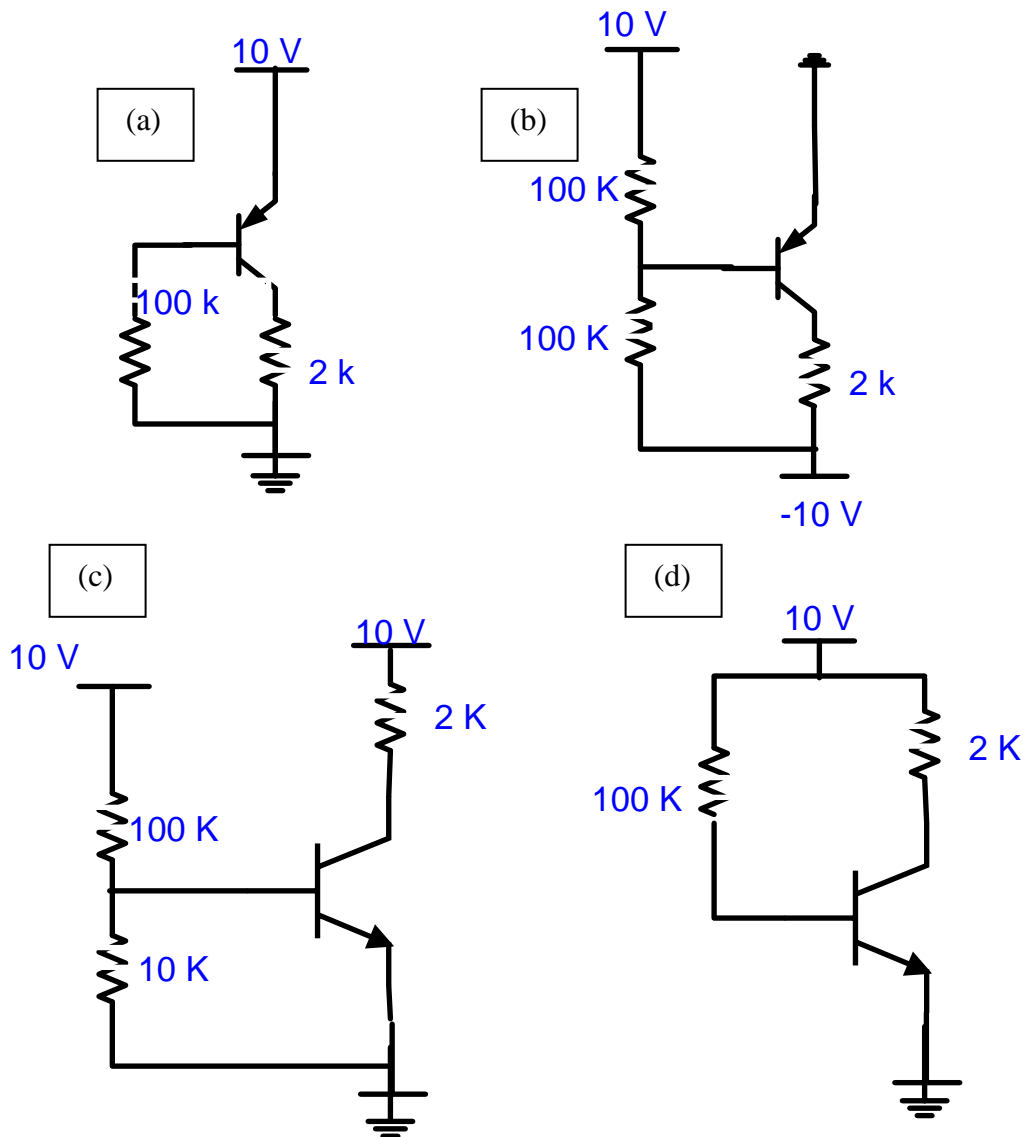
## **Problem 2:**


For the following circuits in which  $V_{BE}$  (or  $V_{EB}$  for PNP transistor) = 0.7 V and  $\beta=10$ . Find the transistor's DC operating point?


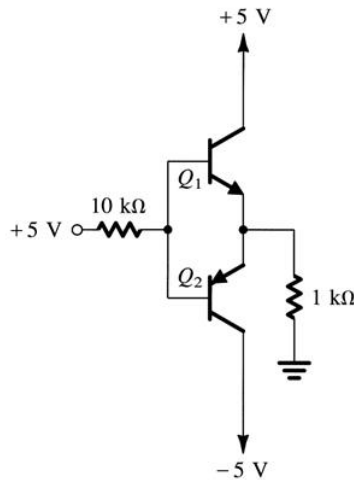
### **Problem 3:**


Evaluate the voltages at all nodes and the currents through all branches.

Assume:  $V_{BE}$  (or  $V_{EB}$  for PNP transistor) = 0.7 V,  $\beta=100$ .


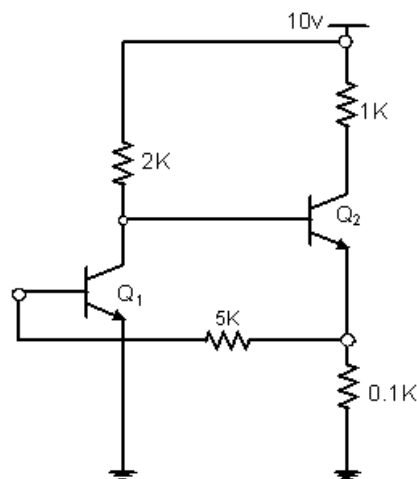
### **Problem 4:**

Evaluate the voltages at all nodes and the currents through all branches. State the DC mode of operation for the transistors. Assume:  $V_{BE}$  (or  $V_{EB}$  for PNP transistor) = 0.7 V  $\beta=50$ .



### **Problem 5**

For the BJT circuit shown,  $R_1=R_2=10\text{k}\Omega$ ,  $V^+=10\text{V}$ ,  $V^-=-2\text{V}$ ,  $R_C=R_E=5\text{k}\Omega$ ,  $R_3=100\text{k}\Omega$ ,  $\beta=100$ .

1. Find the labeled currents  $I_B$ ,  $I_C$ , and  $I_E$ .
2. Calculate  $V_{CE}$
3. What is the DC mode of the transistor?

