



Electronic Circuits for Mechatronics (ELCT 609)

Spring 2021

Lecture 3: BJT Physical Structure & I-V Characteristics


Course Instructor: Dr. Eman Azab



Introduction

- Why we call it Transistor?
 - The name came as an abbreviation of the device job!

Transfer-Resistor

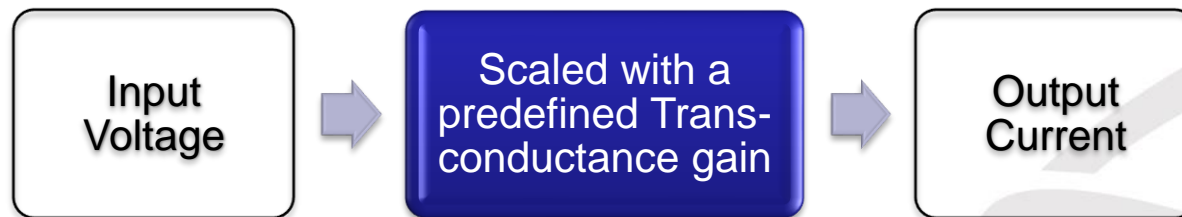




Bipolar Junction Transistor (BJT)

Physical Structure




BJT Physical Structure

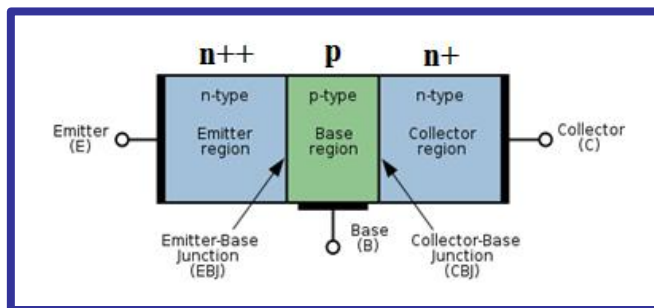- Two back to back PN Junctions
- NPN or PNP Transistor
- Three terminal device, for NPN: Base (**P-Type**), Emitter and Collector (**N-Type**)
 - Base-Emitter Junction (BE-J)
 - Base-Collector Junction (BC-J)
 - Emitter doping is higher than Collector doping



NPN BJT Transistor

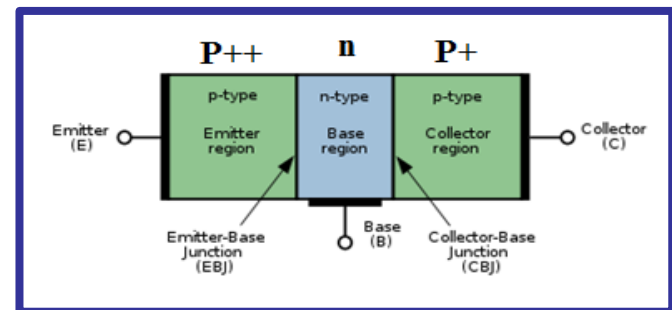

PNP BJT Transistor





BJT Modes of Operation

Electrical Equations of BJT: I-V Characteristics



BJT Circuit Symbol and Structure

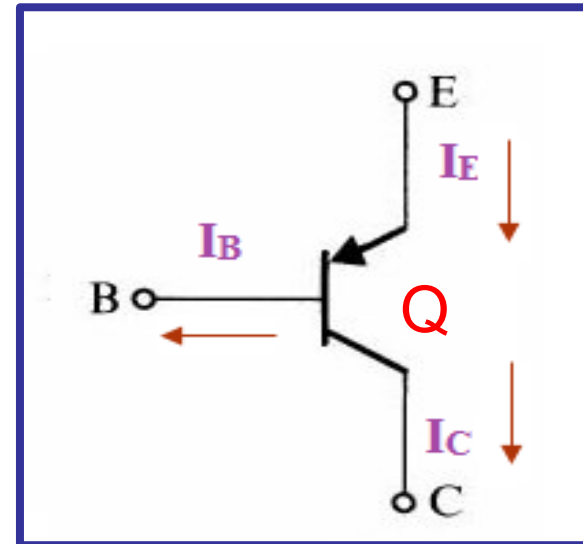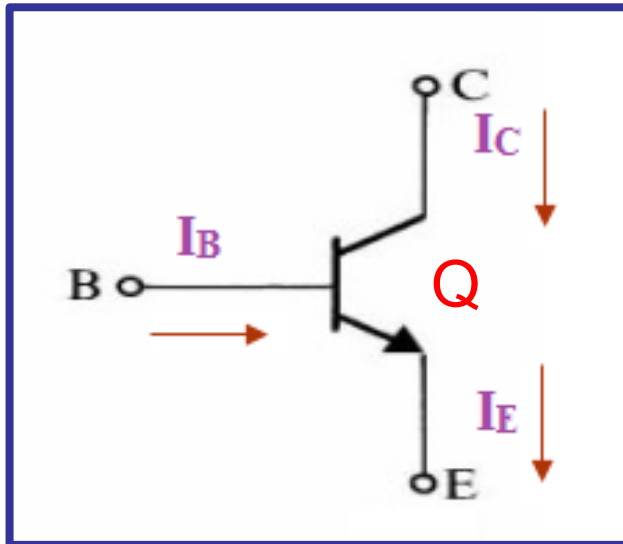




NPN BJT I-V characteristics

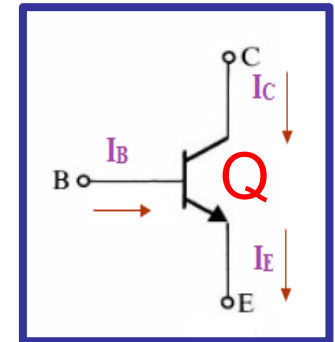1. NPN Transistor in Cutoff Mode

- Base-Emitter Junction is Reverse biased
- Base-Collector Junction is Reverse biased




$$I_C = I_B = I_E = 0$$



NPN BJT I-V characteristics

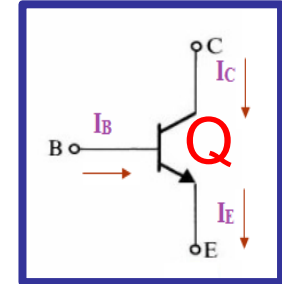2. NPN Transistor in Forward Active Mode

- BE-J is Forward biased & BC-J is reverse biased
- Electrons pass across Base to the collector due to the Base small area (Electrons from the Emitter are collected at the Collector side)






NPN BJT I-V characteristics

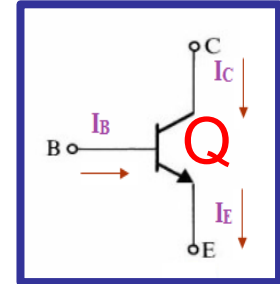2. NPN Transistor in Forward Active Mode (Cont.)

- BE-J is Forward biased & BC-J is reverse biased
- Electrons pass across Base to the collector due to the Base small area (Electrons from the Emitter are collected at the Collector side)
- The transistor's Collector current can be modeled by a **current/voltage dependent current source**
- I_s depends on doping and width of the Base



$$I_C = \beta_F I_B$$



$$I_C = I_s \exp\left(\frac{V_{BE}}{V_T}\right)$$



NPN BJT I-V characteristics

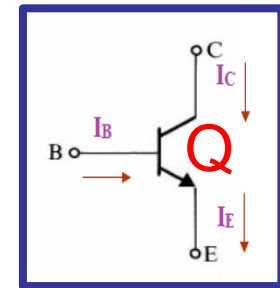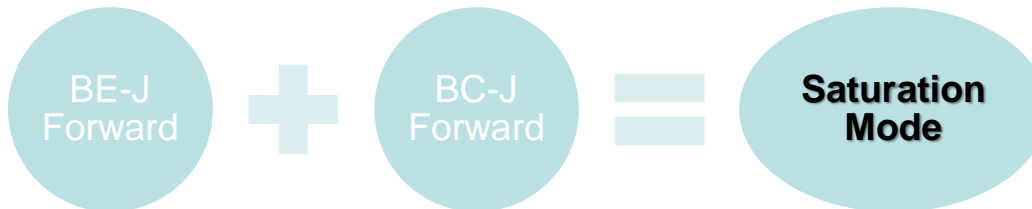3. NPN Transistor in Saturation Mode

- Both junctions are Forward biased
- The total current is the BE-J diffusion current opposite to BC-J diffusion current



- BJT could be used as a closed switch in Saturation

$$V_{BE} \cong 0.7V \quad V_{CE} \cong 0.2V$$


$$V_{BC} \cong 0.5V \quad I_C < \beta_F I_B$$



NPN BJT I-V characteristics

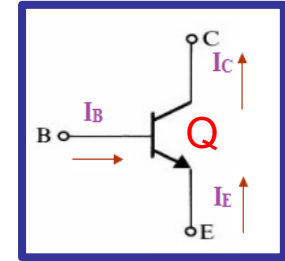4. NPN Transistor in Reverse Active mode

- BC-J is Forward biased
- BE-J Junction is reverse biased
- Emitter and collector reverse their roles
- However, BJT has an asymmetrical physical structure
- The current gain from Base to Emitter is very small




$$V_{BC} \cong 0.5V$$

$$I_E = \beta_R I_B$$

$$\beta_R \ll \beta_F$$



NPN BJT Modes of Operation

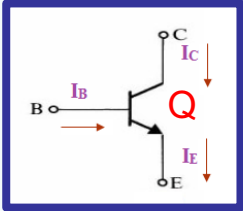Mode	BEJ	BCJ	Equations	Condition
Cutoff	Reverse	Reverse	$I_C = I_E = I_B = 0$	$V_{BE} < 0.7$ $V_{BC} < 0.5$
Active (Forward)		Reverse	$V_{BE} \cong 0.7$ $I_E = I_C + I_B$ $I_C = I_S e^{\frac{V_{BE}}{V_T}}$ $I_C = \beta_F I_B = \alpha_F I_E$ $\alpha_F = \frac{\beta_F}{1 + \beta_F}$	$V_{BC} < 0.5$ Or $V_{CE} > 0.2$
Saturation		Forward	$V_{BE} \cong 0.7$ $V_{BC} \cong 0.5$ $V_{CE} \cong 0.2$ $I_E = I_C + I_B$	$I_C < \beta_F I_B$
Reverse Active	Reverse	Forward	$V_{BC} = 0.5$ $I_C = I_E + I_B$ $I_E = \beta_R I_B = \alpha_R I_C$ $\alpha_R = \frac{\beta_R}{1 + \beta_R}$	$V_{BE} < 0.7$






NPN BJT I-V Characteristics

▪ I_C versus V_{BE} and V_{CE}

$$I_C = I_s \exp\left(\frac{V_{BE}}{V_T}\right)$$


For Active
ONLY

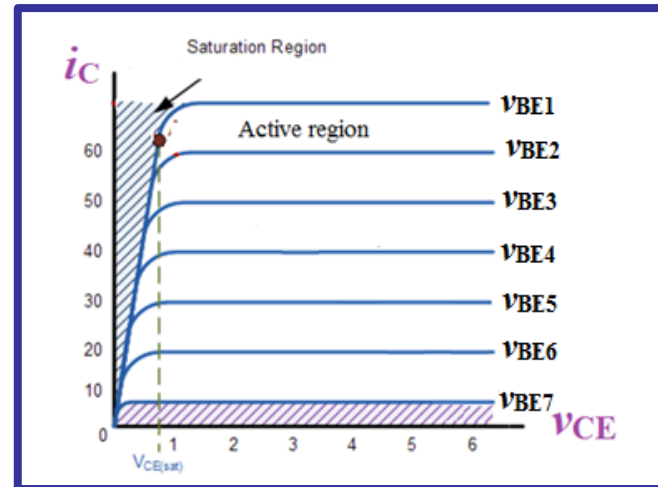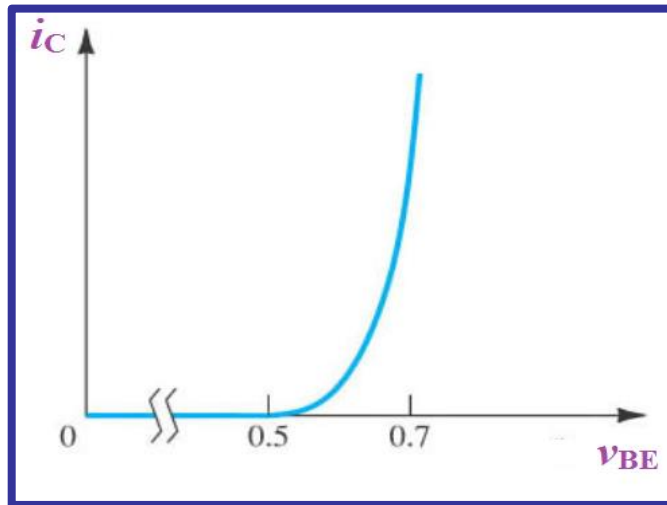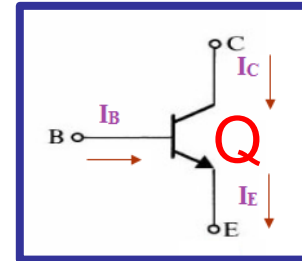



NPN BJT I-V Characteristics

- I_C versus V_{CE}
 - The Early effect

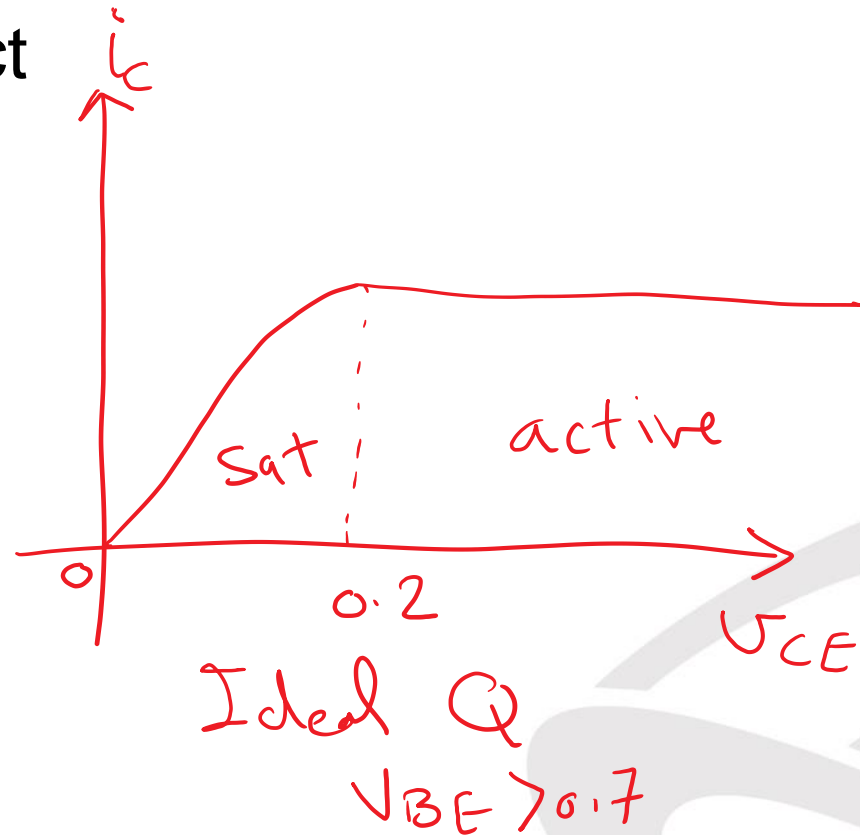




NPN BJT I-V Characteristics

▪ I_C versus V_{CE} (The Early effect)



$$i_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$
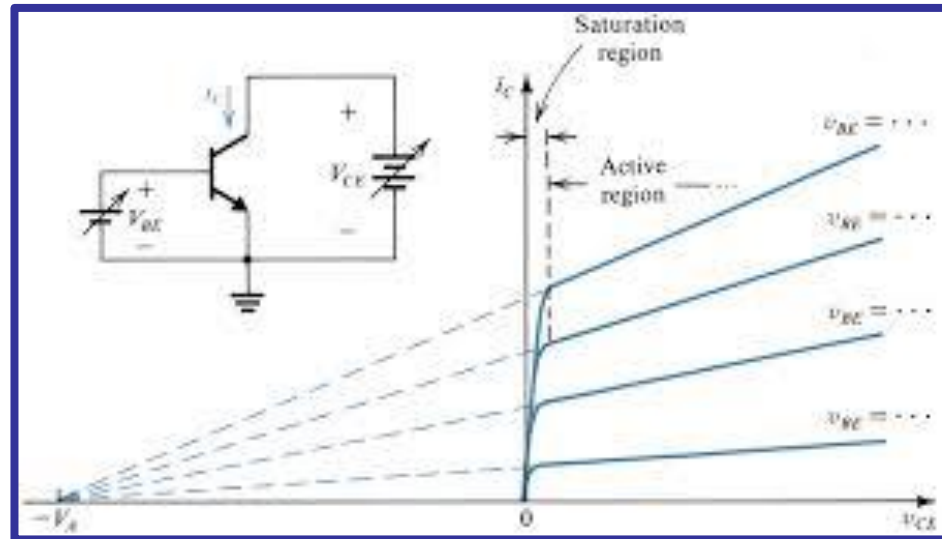
$$r_o = \left(\frac{\partial i_C}{\partial v_{CE}}\right)^{-1} = \frac{V_A}{I_C}$$






BJT Large Signal Model in Active Mode

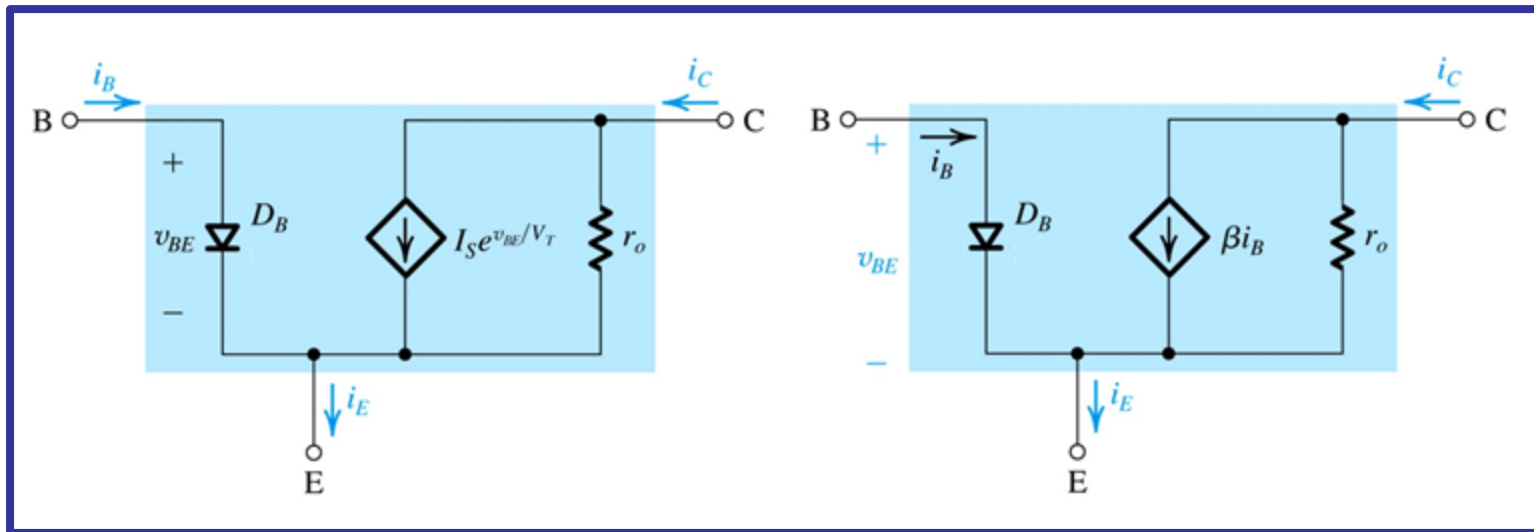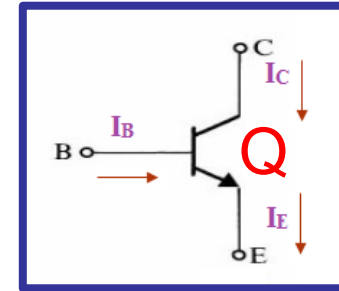



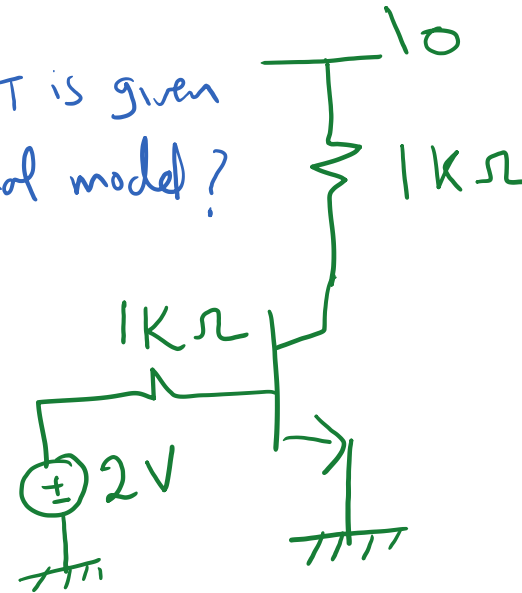Ex: Find I_C , if Q is active
Assume, β_F , V_A , V_T is given
Solve using large signal model?







PNP BJT Physical Structure

▪ BJT PNP Transistor

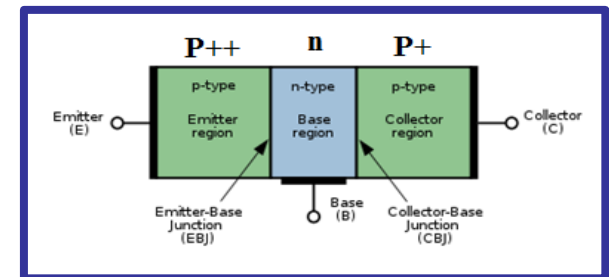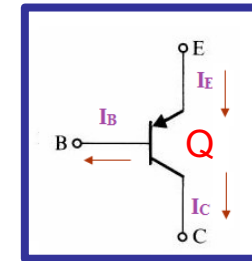- PNP is the NPN Complementary structure
- Two back to back PN Junctions
- Three terminal device: Base (**N-type**), Emitter and Collector (**P-type**)
- Emitter-Base Junction
- Collector-Base Junction
- Emitter doping is higher than Collector doping
- Same modes of operation as NPN Transistor






PNP BJT Transistor






BJT PNP Physical Structure

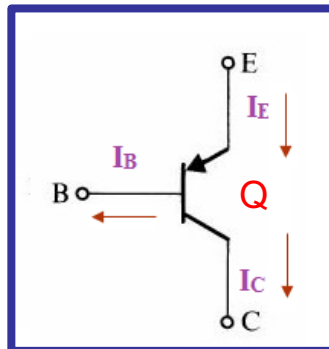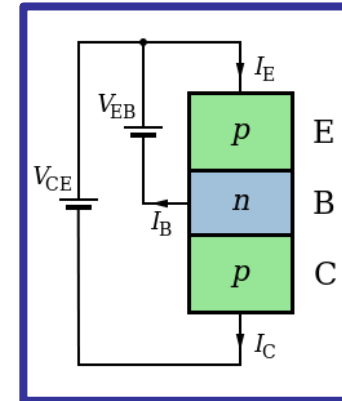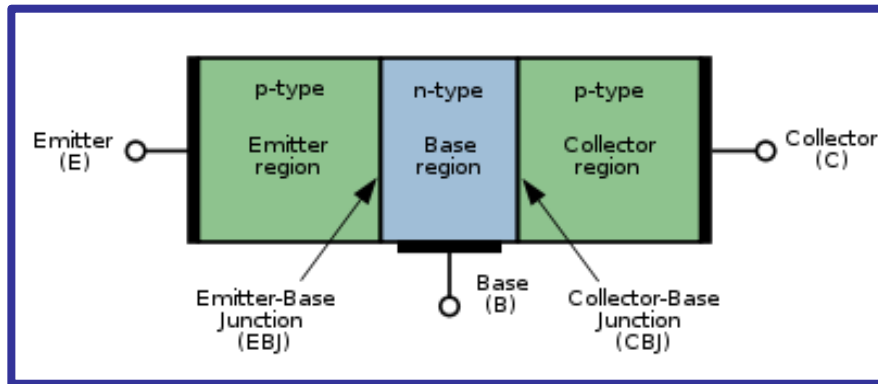■ BJT PNP Transistor in Forward Active Mode





BJT PNP Modes of Operation

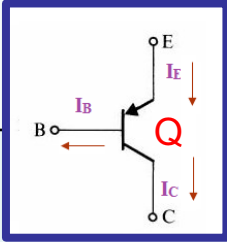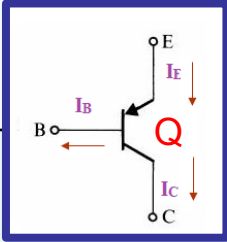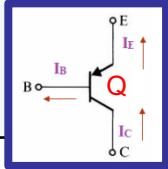Mode	EB-J	CB-J	Equations	Condition
Cutoff	Reverse	Reverse	$I_C = I_E = I_B = 0$	$V_{EB} < 0.7$ $V_{CB} < 0.5$
Active (Forward)	Forward 	Reverse	$V_{EB} \cong 0.7$ $I_E = I_C + I_B$ $I_C = \beta_F I_B = \alpha_F I_E$ $\alpha_F = \frac{\beta_F}{1 + \beta_F}$	$V_{CB} < 0.5$ Or $V_{EC} > 0.2$
Saturation	Forward 	Forward	$V_{EB} \cong 0.7$ $V_{CB} \cong 0.5$ $V_{EC} \cong 0.2$ $I_E = I_C + I_B$	$I_C < \beta_F I_B$
Reverse Active	Reverse 	Forward	$V_{CB} = 0.5$ $I_C = I_E + I_B$ $I_E = \beta_R I_B = \alpha_R I_C$ $\alpha_R = \frac{\beta_R}{1 + \beta_R}$	$V_{EB} < 0.7$



Calculating DC operating point

Solved Exercise




Solved Example

- Find the DC Operating point of the Transistor?

- Given: $V_{BE}=0.7V$, $\beta_F=10$

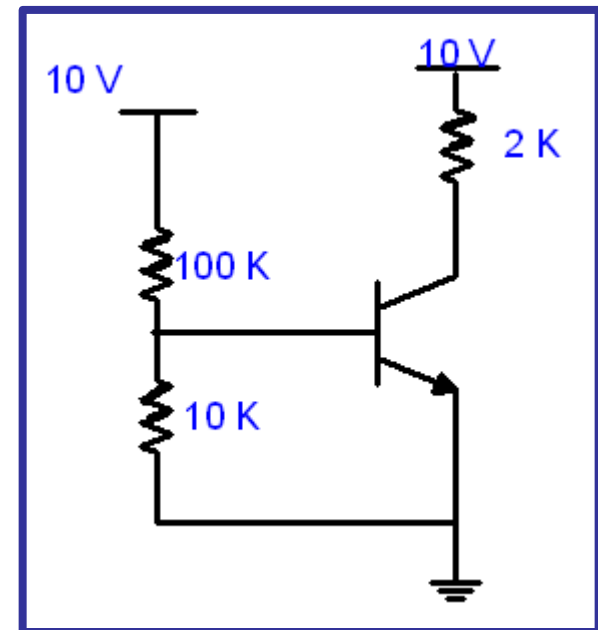(Ans.: $I_B=0.023mA$, $I_C=0.23mA$, $I_E=0.253mA$, $V_{CE}=9.54V$, Active)





DC Analysis of BJT Solution Steps:

1. Identify the BJT Type
2. Place the terminals name on the circuit
3. Write a KVL in the **INPUT Loop**
 - **Input loop** for BJT is any loop containing V_{BE} OR V_{EB}
4. Assume the BJT mode (most of the time active)
5. Calculate the currents and voltages
6. Write KVL in the **OUTPUT loop**
 - **Output loop** for BJT is any loop containing V_{CE} OR V_{EC}
7. **Verify your assumption!**



Example

- Find the DC Operating point of the Transistor?
 - Given: $V_{EB}=0.7V$, $\beta=10$

