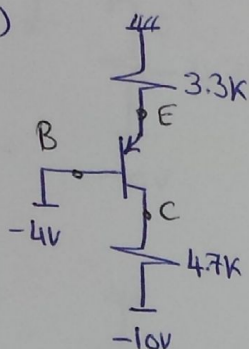


BJT DC Analysis

Problem 1:

$$V_{BE} = V_{EB} = 0.7V, \quad \beta = 50$$

(a)



Assume active:


$$V_B = -4V \rightarrow V_E = -3.3V$$

$$I_E = \frac{0 - (-3.3)}{3.3k} = 1mA, \quad I_B = I_E / (\beta + 1) = 19.6\mu A$$

$$I_C = \beta I_B = 0.98mA \rightarrow V_C = -5.39V$$

$$V_{EC} = 2.09 > 0.2 \rightarrow \text{Assumption correct}$$

(b)

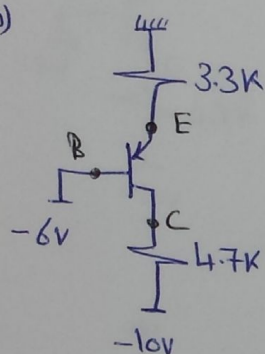

Assume active:

$$V_B = -6V \rightarrow V_E = -5.3V$$

$$I_E = \frac{0 - (-5.3)}{3.3k} = 1.6mA, \quad I_B = 31.5\mu A$$

$$I_C = 1.57mA \rightarrow V_C = -2.6V$$

$$V_{EC} = -5.3 + 2.6 = -2.7 < 0.2V$$


Assumption is wrong. Assume saturation:

$$V_B = -6V, \quad V_E = -5.3V, \quad V_C = -5.5V$$

$$I_C = 0.957mA, \quad I_E = 1.6mA \Rightarrow I_B = 0.64mA$$

$$I_C < \beta I_B \rightarrow \text{Assumption right.}$$

(c)

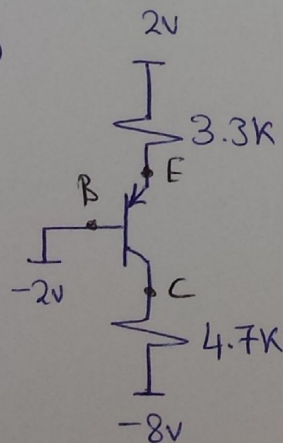


Assume active:

$$V_B = -2V \rightarrow V_E = -1.3V$$

$$I_E = 1mA, \quad I_B = 19.6\mu A$$

$$I_C = 0.98mA, \quad V_C = -3.4V$$
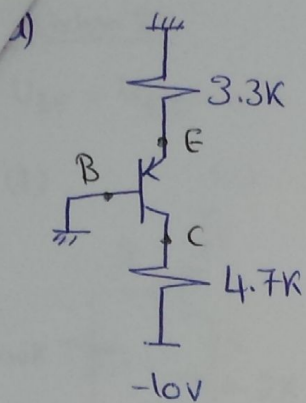
$$V_{EC} = -1.3 + 3.4 = 2.1 > 0.2 \rightarrow \text{Assumption correct}$$




Assume active:

$$U_B = 0 \rightarrow U_E = 0.7V$$

$$I_E = -0.212mA$$

\therefore The transistor is off

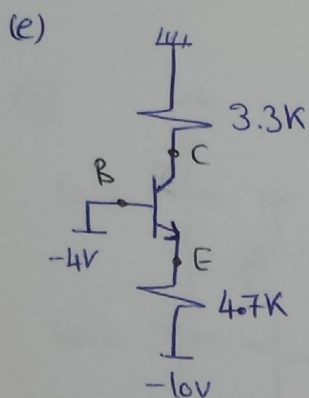

Assume active:


$$U_B = -4V \rightarrow U_E = -4.7V$$

$$I_E = \frac{-4.7 - (-10)}{4.7k} = 1.12mA$$

$$I_B = 22\mu A$$

$$I_C = 1.1mA \rightarrow U_C = -3.64V$$
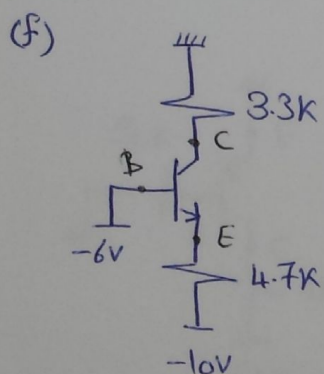
$$V_{CE} = -3.64 - (-4.7) = 1.05 > 0.2V \rightarrow \text{Assumption Correct}$$



Assume active:

$$U_B = -6V \rightarrow U_E = -6.7V$$

$$I_E = 0.7mA \rightarrow I_B = 13\mu A$$


$$I_C = 0.68mA \rightarrow U_C = -2.27V$$

$$V_{CE} = 4.42V > 0.2V \rightarrow \text{Assumption correct}$$

Problem 2:

$$U_{BE} = U_{EB} = 0.7, \quad \beta = 10$$

(a)

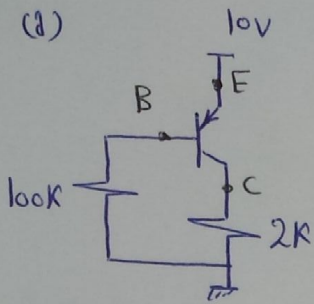

Assume active:


$$U_E = 10V \rightarrow U_B = 9.3V$$

$$I_B = 93\mu A \rightarrow I_C = 930\mu A \rightarrow U_C = 1.86$$


$$I_E = 1.023mA$$

$$V_{EC} = 8.14V > 0.2V \quad \text{Assumption correct}$$

(b)

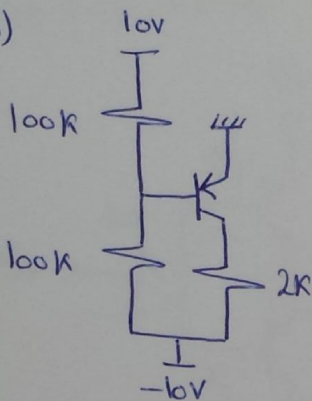

Using Thevenin theory

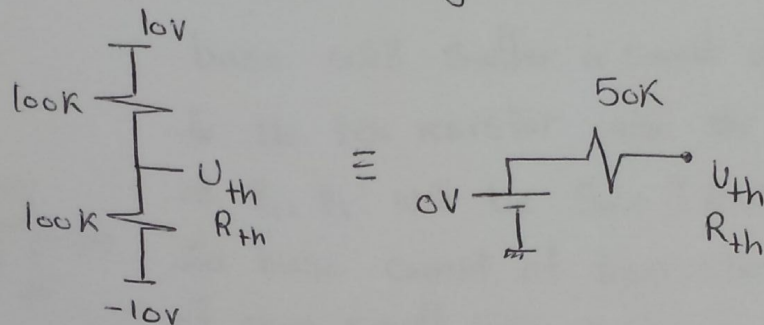


Assume active:

$$U_E = 0 \rightarrow U_B = -0.7V$$


$$I_B = -14\mu A$$

The transistor is off.

(c)

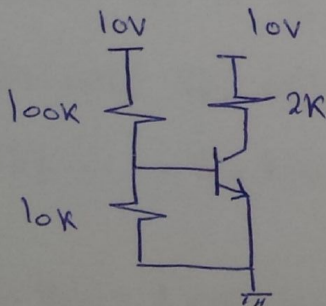

Using Thevenin theory

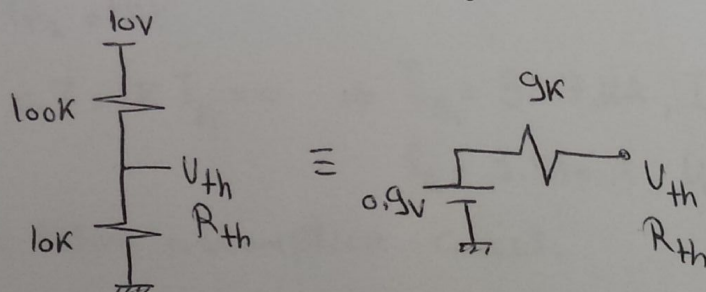


$$U_B = 0.7V \rightarrow I_B = 22\mu A \rightarrow I_C = 220\mu A$$

$$U_C = 9.55V, \quad I_E = 242\mu A$$

$$V_{CE} = 9.55V > 0.2V \rightarrow \text{Assumption correct.}$$

(d)

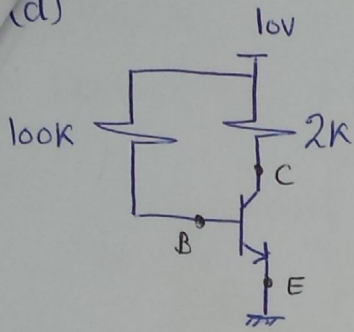

Assume active:


$$U_B = 0.7V \rightarrow I_B = 93\mu A$$

$$I_C = 930\mu A \rightarrow U_C = 8.14V$$

$$U_{CE} = 8.14V > 0.2V \rightarrow \text{Assumption correct.}$$

Problem 3:

$$U_{BE} = U_{EB} = 0.7V, \beta = 100$$

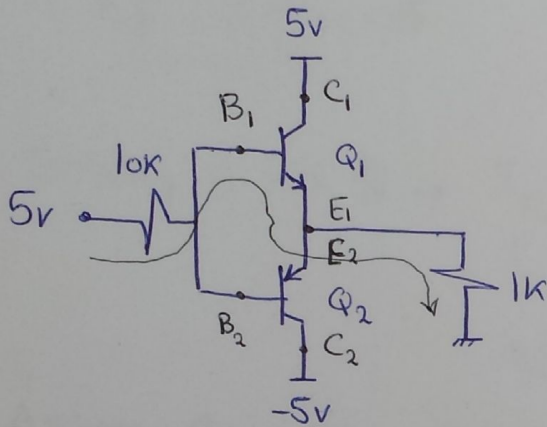

In this problem the 5V supply at base will suffer a small drop due to the 10k resistor and the voltage at B_1, B_2 will be $5V - I(10k)$, with the base current of transistors being of very small value $\Rightarrow U_{B1} = U_{B2} = \underline{5V - \Delta V}$

With that ΔV of very small value $\rightarrow U_{E1} = U_{E2} = 5 - 0.7 - \Delta V$ (measuring from Q_1)
 This will lead to $U_{E1} = U_{E2} = 4.3V - \Delta V$. This requires U_{B2} to be of value $\underline{4.3V - \Delta V - 0.7}$ when going from E_2 to B_2 and that isn't what we actually measured at start! This means there must be either Q_1 or Q_2 off.

Assume Q_1 active, Q_2 off:

$$\text{KVL: } -5 + 10k I_{B1} + 0.7 + 1k I_{E1} = 0 \Rightarrow I_{B1} = 38.7\mu A, I_{C1} = 3.87mA$$


$$I_{E1} = 3.91mA, U_{E1} = 3.9V, U_{B1} = 4.6V$$

$$\therefore U_{CE1} = 1.08V > 0.2V \rightarrow \text{Active assumption correct.}$$

$$\therefore U_{EB2} = 3.9 - 4.6 = -0.7V \rightarrow \text{off assumption correct.}$$

Problem 4:

$$V_{BE} = 0.7V, \beta = 50$$

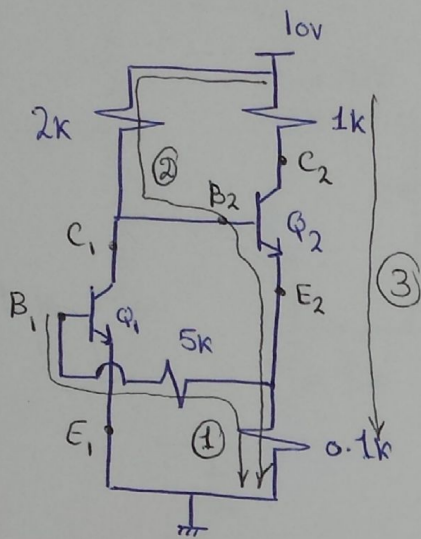

Assume Q_1, Q_2 active:

KVL @ loop 1:

$$-0.7 - 5kI_{B1} + 0.1k(I_{E2} - I_{B1}) = 0$$

$$-4.9kI_{B1} + 0.1kI_{E2} = 0.7 \rightarrow (1)$$

KVL @ loop 2:

$$-10 + 2k(I_{C1} + I_{B2}) + 0.7 + 0.1k(I_{E2} - I_{B1}) = 0$$

$$99.9kI_{B1} + 0.14I_{E2} = 9.3 \rightarrow (2)$$

Solving (1) and (2) $\rightarrow I_{E2} = 10.8mA, I_{B1} = 77.9\mu A$

$$I_{C2} = 10.6mA$$

$$V_{C2} = -0.6V \rightarrow Q_2 \text{ is not active}$$

Assume Q_1 active, Q_2 saturation:

from KVL loop (2) $\rightarrow 99.9kI_{B1} + 2kI_{B2} + 0.1I_{C2} + 0.1I_{B2} = 9.3$

$$99.9kI_{B1} + 2.1kI_{B2} + 0.1I_{C2} = 9.3 \rightarrow (3)$$

KVL @ loop 3:

$$-10 + I_{C2}(1k) + 0.2 + 0.1k(I_{E2} - I_{B1}) = 0$$

$$1kI_{C2} + 0.1kI_{C2} + 0.1kI_{B2} - 0.1kI_{B1} = 10$$

$$1.1kI_{C2} + 0.1kI_{B2} - 0.1kI_{B1} = 10 \rightarrow (4)$$


Solving (1), (3), (4) $\rightarrow I_{B1} = 62.14\mu A, I_{C1} = 3.104mA, I_{E1} = 3.17mA$

$$I_{B2} = 1.04mA, I_{C2} = 9.96mA, I_{E2} = 10.04mA$$



$$V_{C1} = 1.712V, V_{B1} = 0.7V, V_{E1} = 0V \rightarrow V_{CE1} > 0.2V \text{ Assumption right}$$

$$V_{C2} = 1V, V_{B2} = 1.71V, V_{E2} = 1V \rightarrow I_{C2} < \beta I_{B2} \text{ Assumption right}$$

Problem 5: ($\beta=100$)

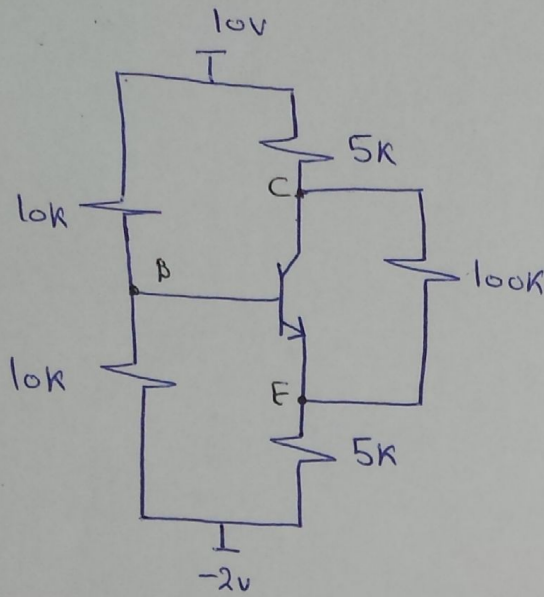

Using Thevenin:

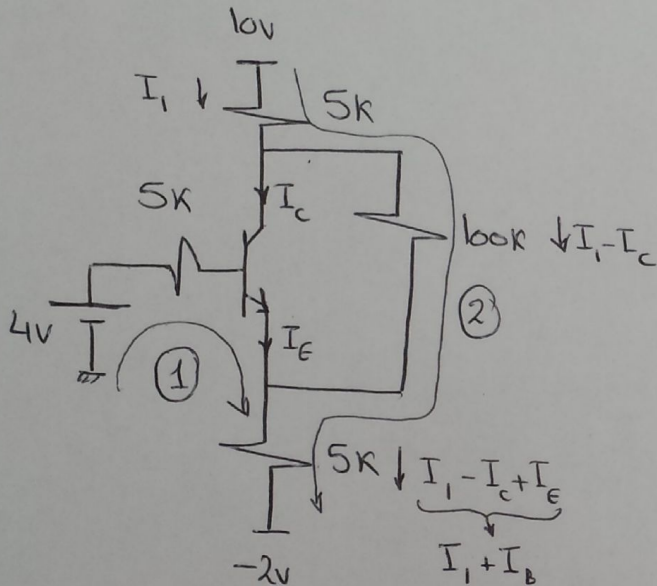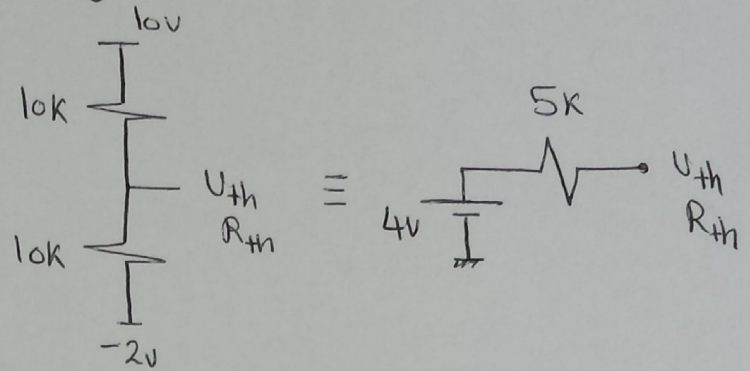

KVL @ loop 1:

$$-4 + 5k I_B + 0.7 + 5k(I_1 + I_B) = 2 \rightarrow (1)$$

KVL @ loop 2

$$-10 + 5k I_1 + 100k(I_1 - I_C) + 5k(I_1 + I_B) = 2 \rightarrow (2)$$

Solving (1), (2)

$$I_1 = 1.04 \text{ mA}, I_B = 10.2 \mu\text{A}, I_C = 1.02 \text{ mA}$$

$$V_C = 4.8 \text{ V}, V_E = 3.25 \text{ V}$$

$$V_{CE} = 1.55 \text{ V} > 0.2 \text{ V}$$

Assumption correct.