



Electronic Circuits for Mechatronics (ELCT 609)

Spring 2021

Lecture 6: BJT Amplifiers Configurations

Course Instructor: Dr. Eman Azab



BJT Amplifier Configurations

Basic Configurations and their Characteristics



Analysis of BJT Amplifiers

- ❑ **Objective:** Calculate the **Voltage gain**, **Input Resistance** and **Output Resistance**
- ❑ **Solution Steps:**
 1. DC Analysis: Determine the DC operating Point (Deactivate AC signals & All External Capacitors impedances are considered open Circuit)
 2. Calculate the small signal model parameters: g_m , r_π
 3. Replace the BJT with its small signal model (DC sources are deactivated & All External Capacitors impedances are considered Short Circuit) (AC Analysis)
 4. Analyze the circuit to calculate the voltage gain, Input and Output Resistances

Common Emitter Amplifier

- **Objective:** Calculate the voltage gain, Input and Output Resistances
 - Input terminal **Base**
 - Output Terminal **Collector**



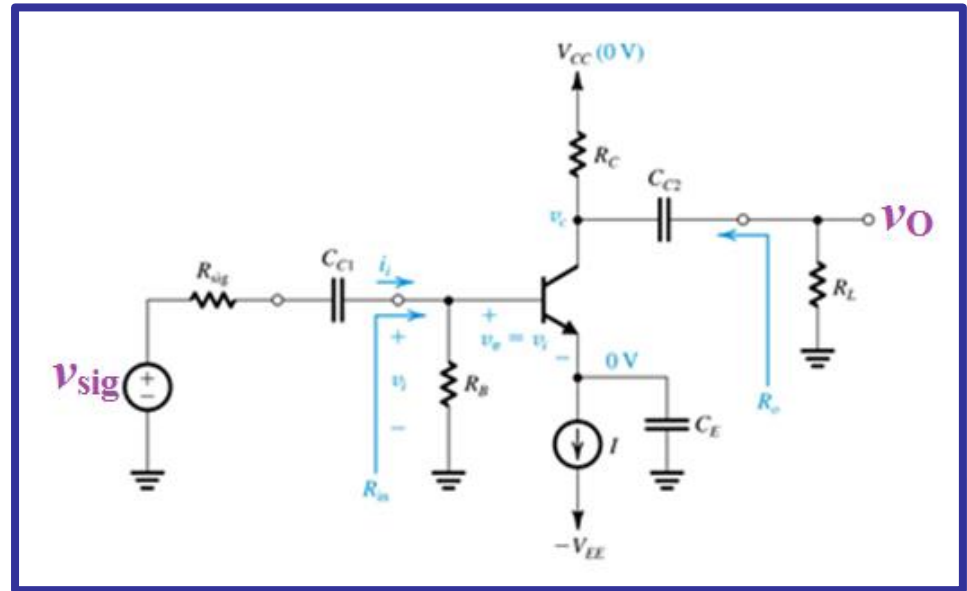
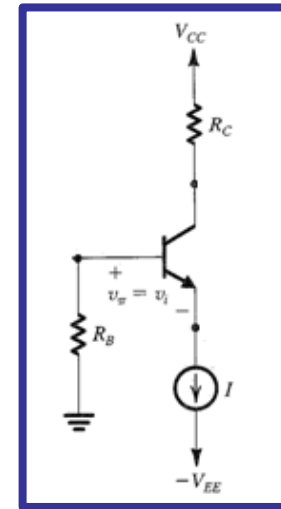


Figure from Sedra/Smith, Copyright © 2010 by Oxford University Press, Inc.

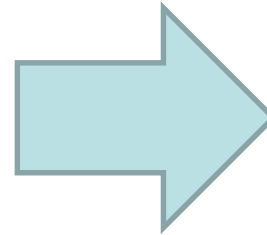

Common Emitter Amplifier

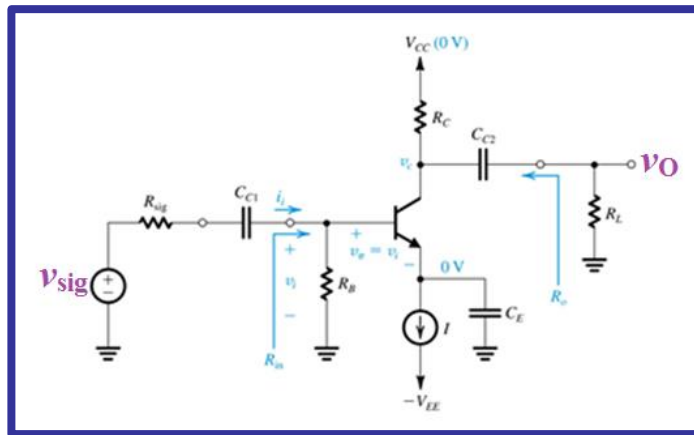1. Calculate the DC Current (DC Analysis)






2. Calculate g_m and r_{π}

$$I_C = \frac{\beta}{1 + \beta} I \cong I$$



Common Emitter Amplifier

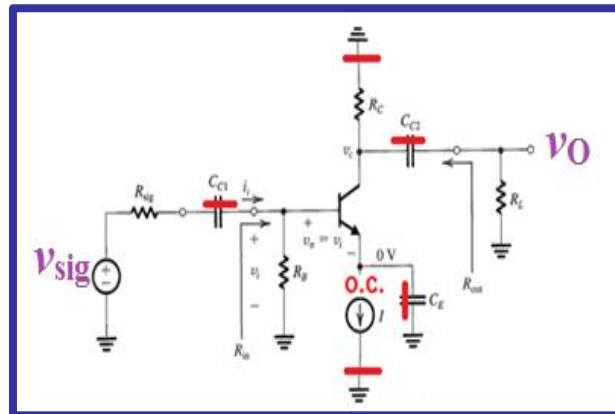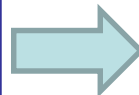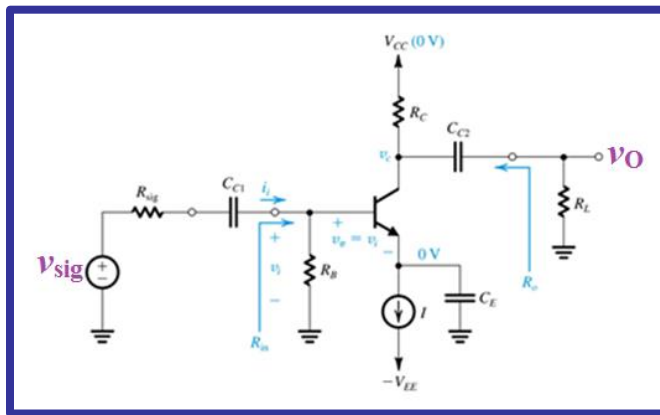
3. AC Analysis: Draw the equivalent small signal model (Include r_o if given)





Common Emitter Amplifier


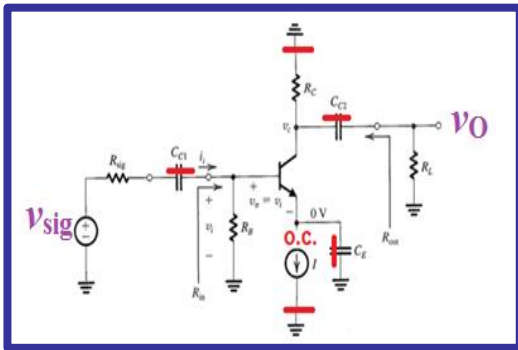
3. **AC Analysis: Draw the equivalent small signal model** (Include r_o if given)
4. **Calculate the gain, input and output Resistance**





Common Emitter Amplifier

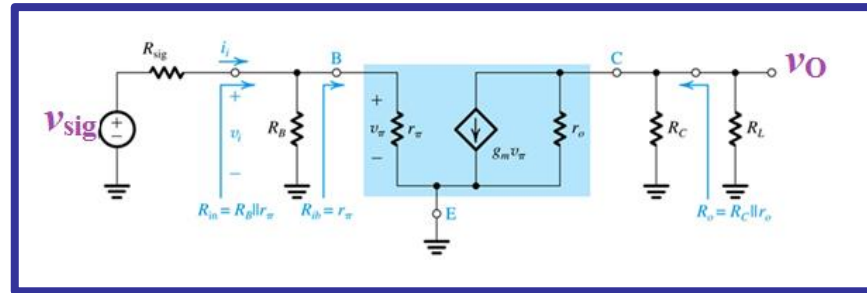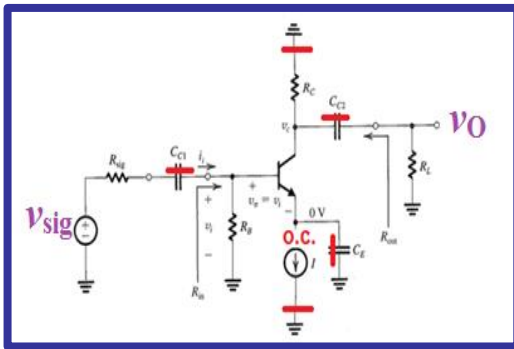- Calculate the gain, input and output Resistance



$$A_v = \frac{v_O}{v_{sig}} = -g_m (r_o // R_C // R_L) \frac{R_B // r_{\pi}}{R_B // r_{\pi} + R_{sig}}$$

$$R_{in} = R_B // r_{\pi}$$

$$R_{out} = r_o // R_C // R_L$$




Common Emitter Amplifier

- **Notes on Common Emitter Configuration:**
 - **Inverting Amplifier**
 - **Modulus of Gain is greater than one**
 - **High Input Resistance**
 - **High Output Resistance**



Common Base Amplifier

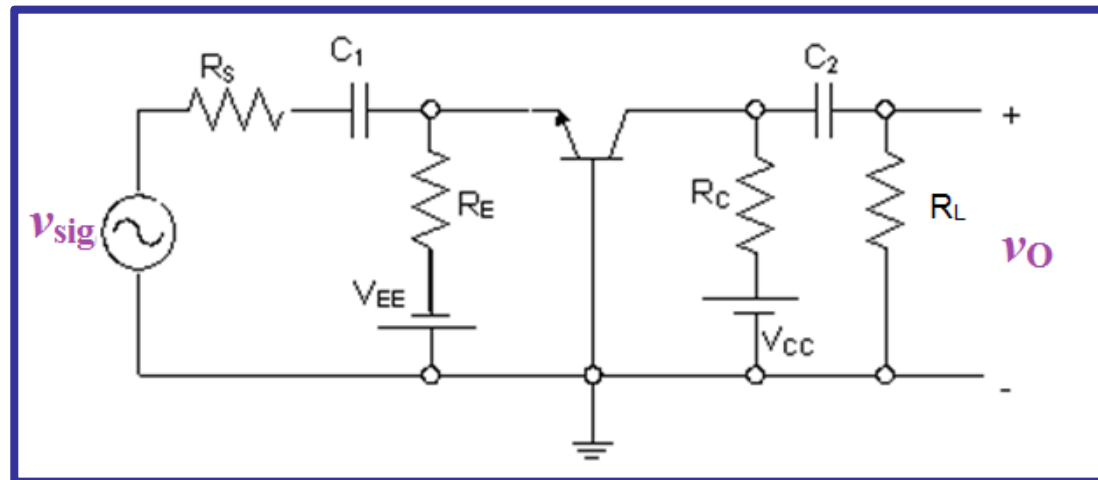
- **Objective:** Calculate the voltage gain, Input and Output Resistances
 - Input terminal **Emitter**
 - Output Terminal **Collector**





Common Base Amplifier


▪ Step 1: DC Analysis

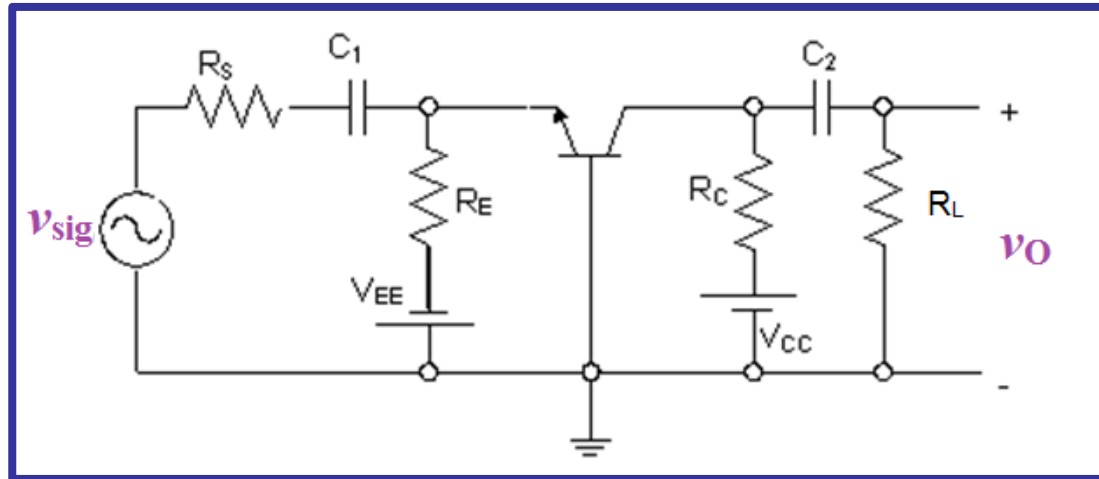



Common Base Amplifier


- Step 2 : Draw small signal model

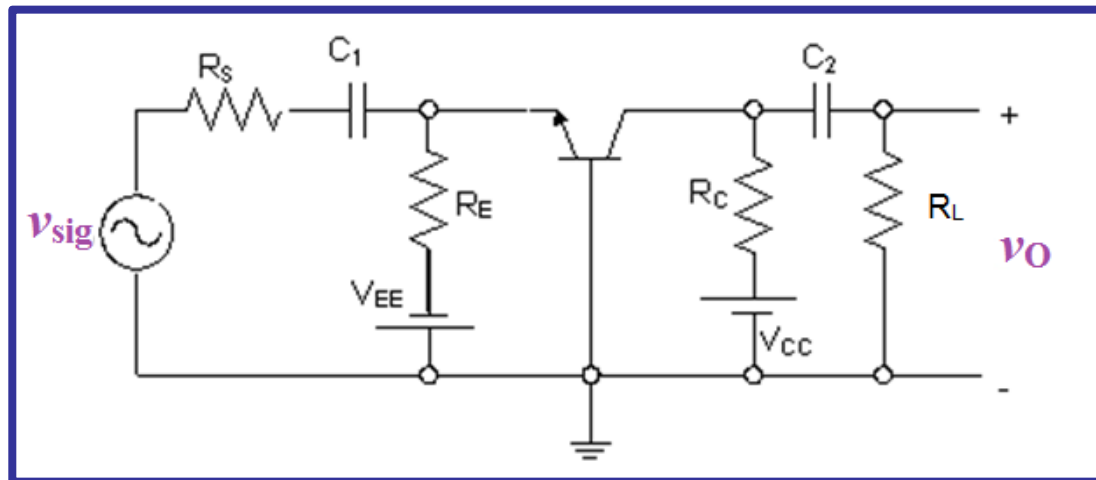



Common Base Amplifier

- Voltage gain (r_o is neglected)

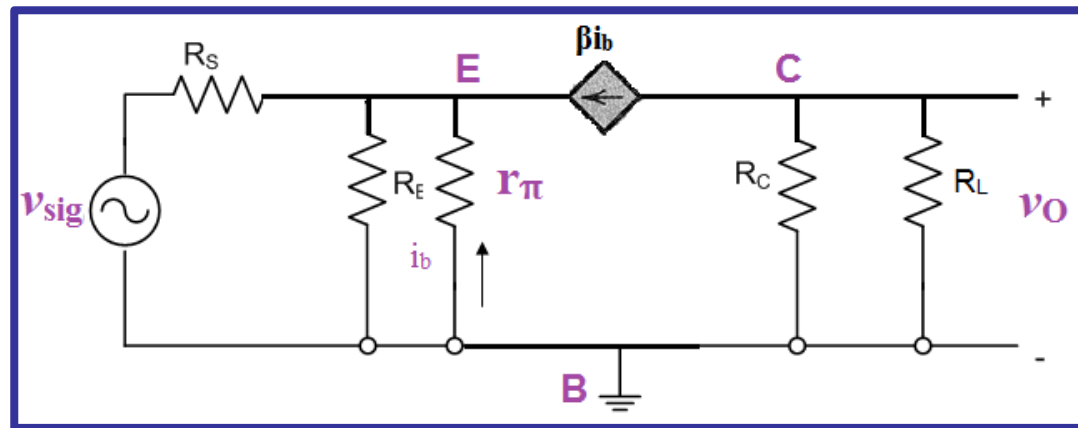


$$A_v = \frac{v_O}{v_{sig}} = \frac{g_m(R_C // R_L)}{1 + \frac{R_S}{(R_E // \frac{r_\pi}{1 + \beta})}}$$



Common Base Amplifier

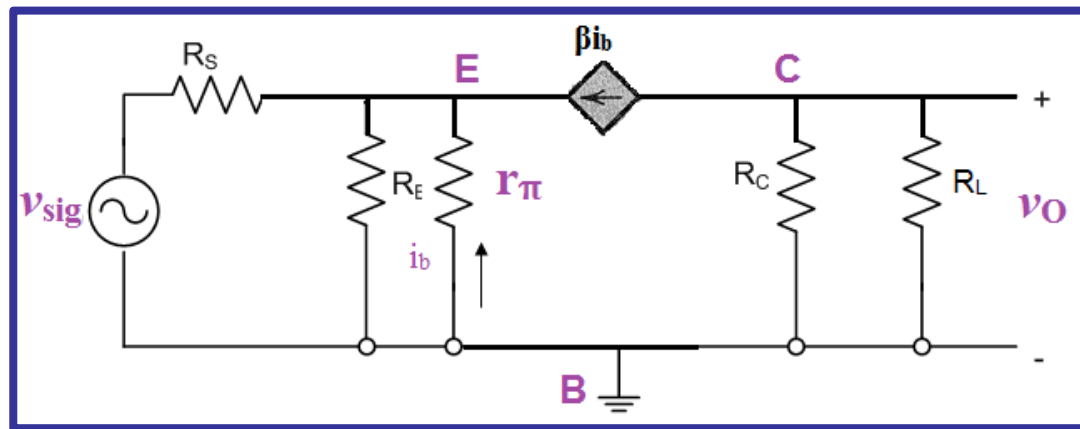- Input and Output Resistance (r_o is neglected)



$$R_{in} = R_S + (R_E // \frac{r_{\pi}}{1 + \beta})$$

$$R_{out} = R_C // R_L$$




Common Base Amplifier

- **Notes on Common Base Configuration:**
 - **Non-Inverting Amplifier**
 - **Gain is greater than unity**
 - **Low Input Resistance**
 - **High Output Resistance**



Common Collector Amplifier

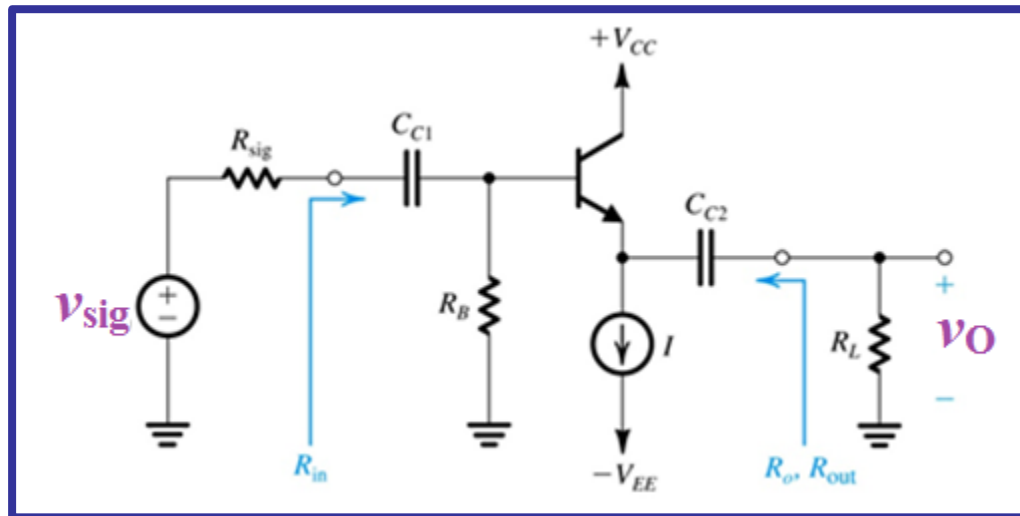
- **Objective:** Calculate the voltage gain, Input and Output Resistances
 - Input terminal **Base**
 - Output Terminal **Emitter**





Common Collector Amplifier


- Step 1 and 2:

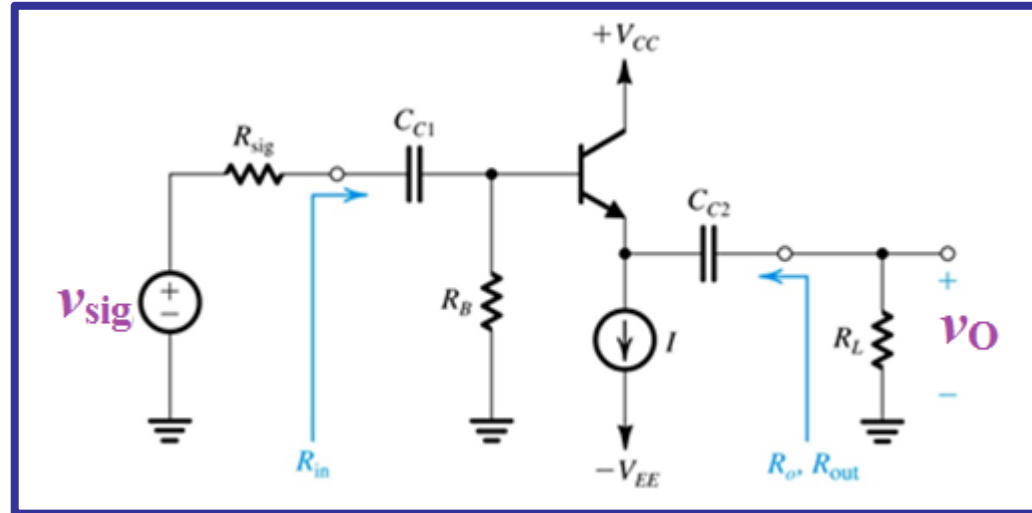



Common Collector Amplifier

- Voltage gain

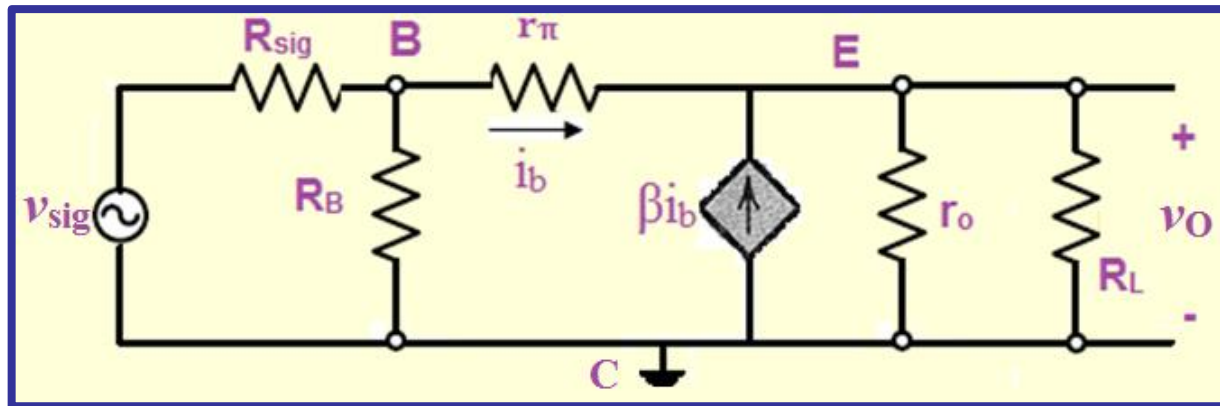


$$A_v = \frac{v_O}{v_{sig}} = \frac{(1 + \beta) (r_o // R_L)}{(r_{\pi} + (1 + \beta) (r_o // R_L)) \left(1 + \frac{R_{sig}}{R_B}\right) + R_{sig}}$$



Common Collector Amplifier

□ Input and Output Resistance

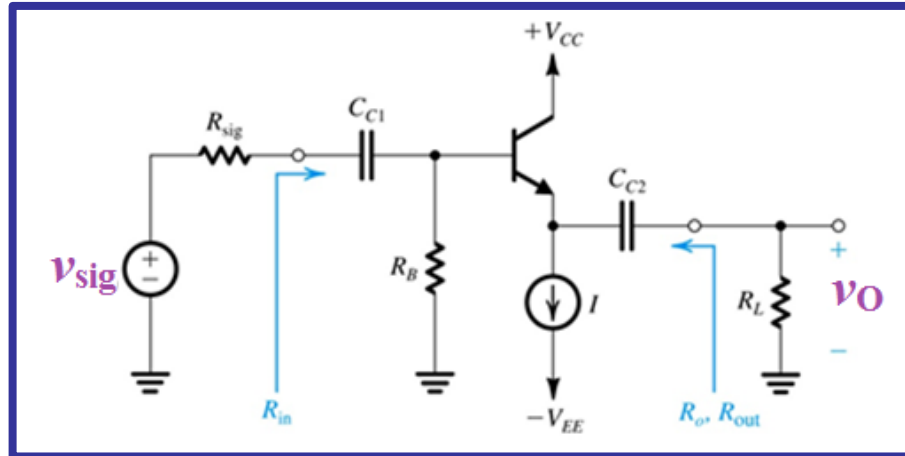

$$R_{in} = R_B // (r_{\pi} + (1 + \beta)(r_o // R_L))$$

$$R_{out} = r_o // \left(\frac{r_{\pi} + (R_B // R_{sig})}{1 + \beta} \right)$$



Common Collector Amplifier

- **Notes on Common Collector Configuration:**
 - **Non-Inverting Amplifier**
 - **Gain is less than unity**
 - **Source Follower (Buffer)**
 - **High Input Resistance**
 - **Low Output Resistance**



Common Emitter with emitter Resistance

Exercise:

- Find the Voltage gain, input and Output Resistance

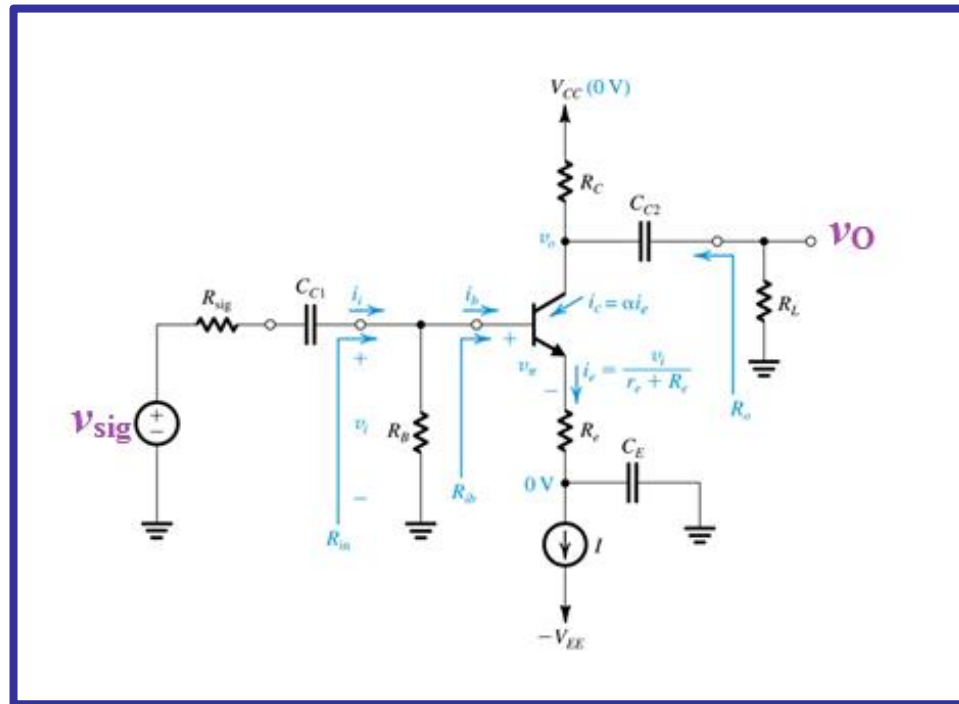


Figure from Sedra/Smith, Copyright © 2010 by Oxford University Press, Inc.