

Mechatronics Engineering



ADC and DAC Programming in AVR

Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Materials Science
German University in Cairo



Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Analog vs. Digital Signals

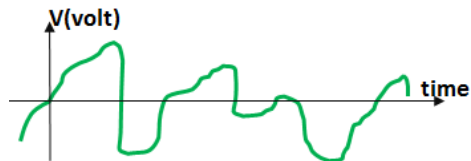
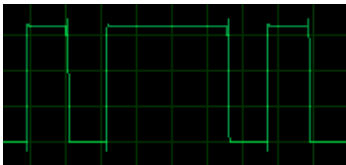


Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

DAC


$$\text{Step size} = \frac{V_{\text{REF}}}{\text{Num of steps}}$$
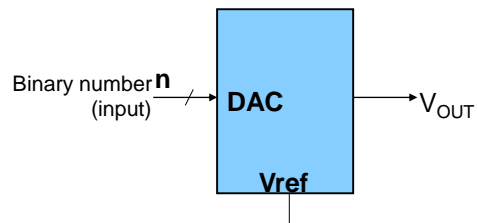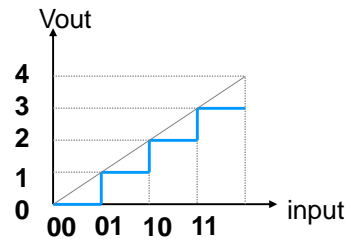
$$V_{\text{OUT}} = \text{num} \times \text{step size}$$



Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Connecting a DAC to the microcontroller

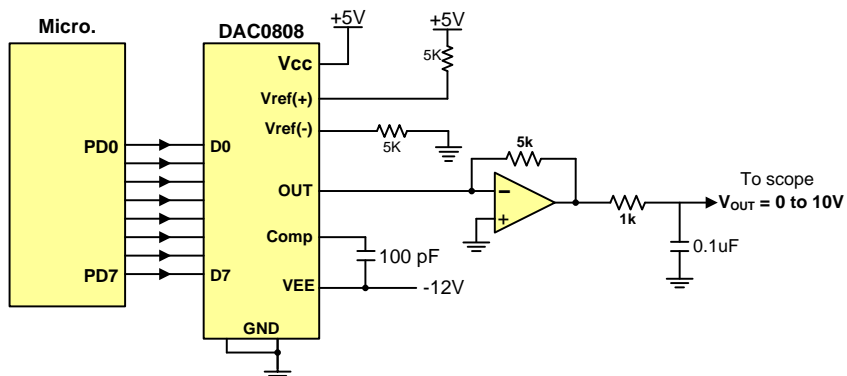


Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Generating a saw-tooth wave using DAC

```
#include <avr/io.h>

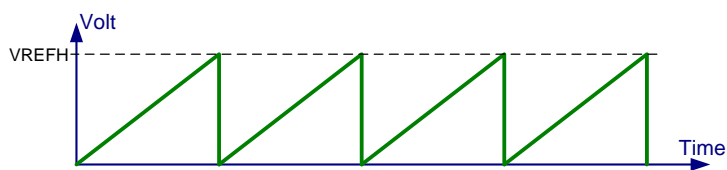int main (void)
{
    unsigned char i = 0; //define a counter
    DDRD = 0xFF; //make Port D an output
    while (1) //do forever
    {
        PORTD = i; //copy i into PORTD to be converted
        i++; //increment the counter
    }
}
```





Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

ADC


$$\text{stepSize} = \frac{V_{\text{ref}}}{\text{numofsteps}}$$
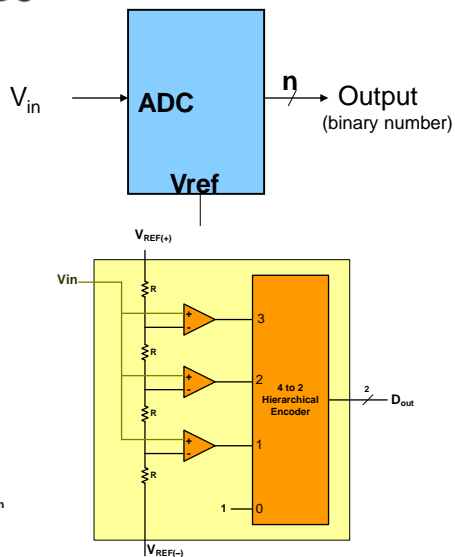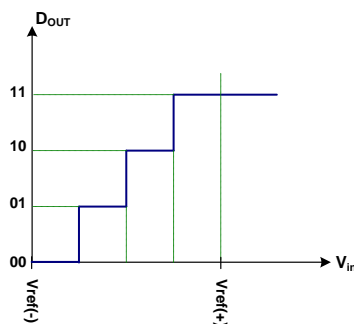
$$\text{output} = \left\lfloor \frac{V_{\text{in}}}{\text{stepSize}} \right\rfloor$$




Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Successive Approximation ADC

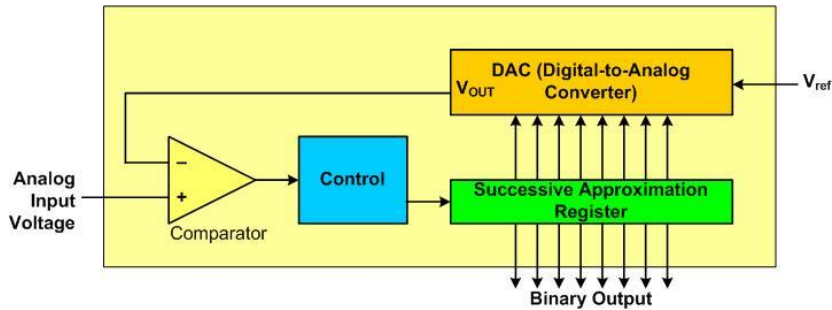

Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

ADC in AVR

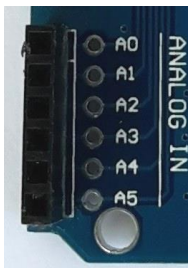


		28 pin	
(PCINT14/RESET) PC6	1	28	PC5 (ADC5/SCL/PCINT13)
(PCINT16/RXD) PD0	2	27	PC4 (ADC4/SDA/PCINT12)
(PCINT17/TXD) PD1	3	26	PC3 (ADC3/PCINT11)
(PCINT18/INT0) PD2	4	25	PC2 (ADC2/PCINT10)
(PCINT19/OC2B/INT1) PD3	5	24	PC1 (ADC1/PCINT9)
(PCINT20/XCK/T0) PD4	6	23	PC0 (ADC0/PCINT8)
VCC	7	22	GND
GND	8	21	AREF
(PCINT6/XTAL1/TOSC1) PB6	9	20	AVCC
(PCINT7/XTAL2/TOSC2) PB7	10	19	PB5 (SCK/PCINT5)
(PCINT21/OC0B) PD5	11	18	PB4 (MISO/PCINT4)
(PCINT22/OC0A/AIN0) PD6	12	17	PB3 (MOSI/OC2A/PCINT3)
(PCINT23/AIN1) PD7	13	16	PB2 (SS/OC1B/PCINT2)
(PCINT0/CLKO/ICP1) PB0	14	15	PB1 (OC1A/PCINT1)




Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

ADC in AVR

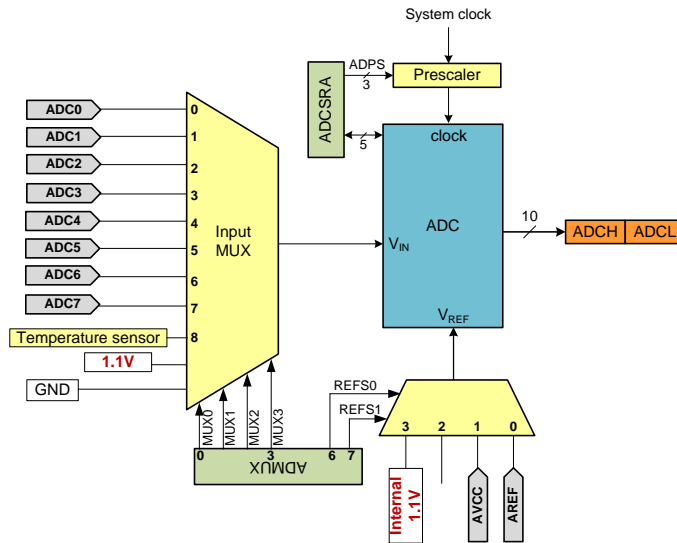


Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

ADMUX

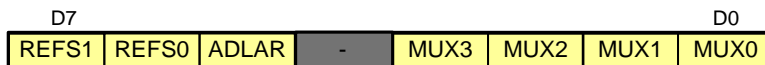

- MUX0-MUX1: input select
- ADLAR:

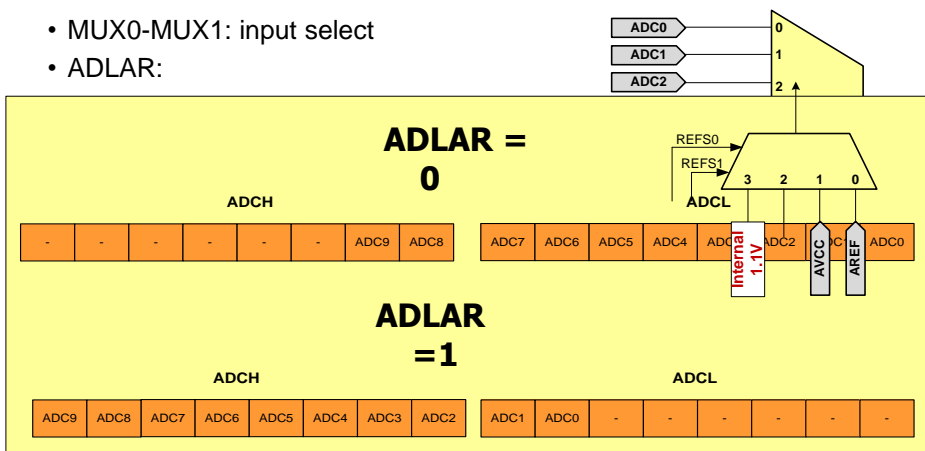

Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

ADCSA

ADEN	ADSC	ADATE	ADIF	ADIE	ADPS2	ADPS1	ADPS0
------	------	-------	------	------	-------	-------	-------

ADEN- Bit7 ADC Enable

This bit enables or disables the ADC. Writing this bit to one will enable and writing this bit to zero will disable the ADC even while a conversion is in progress.

ADSC- Bit6 ADC Start Conversion

To start each conversion you have to write this bit to one.

ADATE- Bit5 ADC Auto Trigger Enable

Auto Triggering of the ADC is enabled when you write this bit to one.

ADIF- Bit4 ADC Interrupt Flag

This bit is set when an ADC conversion completes and the Data Registers are updated

ADIE- Bit3 ADC Interrupt Enable

Writing this bit to one enables the ADC Conversion Complete Interrupt.

ADPS2:0- Bit2:0 ADC Prescaler Select Bits

These bits determine the division factor between the XTAL frequency and the input clock to the ADC.



Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

ADC Prescaler

- PreScaler Bits let us change the clock frequency of ADC
- The frequency of ADC should not be more than 200 KHz
- Conversion time is longer in the first conversion

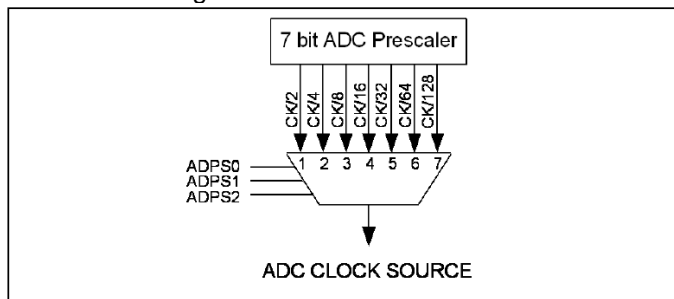


Table 13-3: V_{ref} source selection table

Condition	Sample and Hold Time (Cycles)	Conversion Time (Cycles)
First Conversion	14.5	25
Normal Conversion, Single ended	1.5	13
Normal Conversion, Differential	2	13.5
Auto trigger conversion	1.5 / 2.5	13/14



Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Steps in programming ADC

1. Make the pin for the selected ADC channel an input pin.
2. Turn on the ADC module
3. Select the conversion speed
4. Select voltage reference and ADC input channels.
5. Activate the start conversion bit by writing a one to the ADSC bit of ADCSRA.
6. Wait for the conversion to be completed by polling the ADIF bit in the ADCSRA register.
7. After the ADIF bit has gone HIGH, read the ADCL and ADCH registers to get the digital data output.
8. If you want to read the selected channel again, go back to step 5.
9. If you want to select another Vref source or input channel, go back to step 4.



Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

A program with ADC

- This program gets data from channel 0 (ADC0) of ;ADC and displays the result on Port B and Port D.

```
#include <avr/io.h>
#define F_CPU 16000000UL
#include <util/delay.h>

int main (void)
{
    DDRB = 0xFF; //make Port B an output
    DDRD = 0xFF; //make Port D an output

    ADCSRA= 0x87; //make ADC enable and select ck/128
    ADMUX= 0xC8; //1.1V Vref, temp. sensor, right-justified

    while(1)
    {
        ADCSRA |= (1<<ADSC); //start conversion

        while((ADCSRA&(1<<ADIF))==0); //wait for conversion to finish

        ADCSRA |= (1<<ADIF);

        PORTD = ADCL; //give the low byte to PORTD
        PORTB = ADCH; //give the high byte to PORTB

        _delay_ms(100);
    }
}
```



Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Sensors


- Sensor: Converts a physical signal (e.g. light, temperature, humidity, etc.) to an electrical signal (e.g. resistance, voltage, current, capacitance, etc)




Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

LM35 & LM34 (Temperature Sensors)

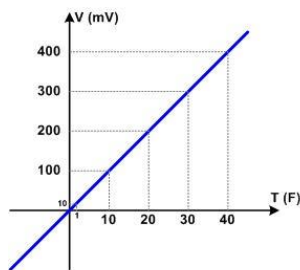- LM35 and LM34:
 - convert temp. to voltage
 - 10mV for each degree



(a) LM34

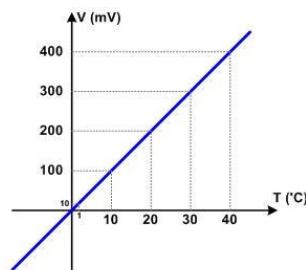


(b) LM35

Bottom view
TO92 Package



Top view
TO220 Package

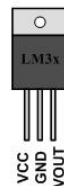


Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Using LM35

```
//this program reads the sensor and displays it on Port B and D
#include <avr/io.h> //standard AVR header
int main (void)
{
    DDRB = 0xFF; //make Port B an output
    DDRD = 0xFF; //make Port D an output
    DDRC = 0; //make Port C an input for ADC input
    ADCSRA = 0x87; //make ADC enable and select ck/128
    ADMUX = 0xC0; //1.1V Vref, ADC0, right-justified


    while (1){
        ADCSRA |= (1<<ADSC); //start conversion
        while((ADCSRA&(1<<ADIF))==0); //wait for end of conversion
        ADCSRA |= (1<<ADIF); //clear the ADIF flag
        PORTD = ADCL;
        PORTB = ADCH;
    }
}
```

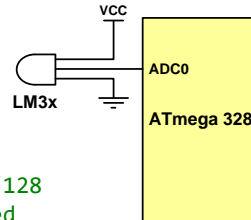

Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Thermistor (a temperature sensor)

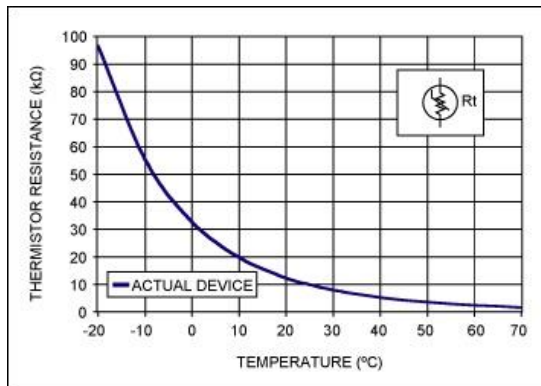- Converts temperature to resistance
- It is not linear



Prof. Ayman A. El-Badawy
Department of Mechatronics Engineering
Faculty of Engineering and Material Science

Signal conditioning

- The output of some sensors (e.g. PT100) is in form of resistance
- Some humidity sensor provide the result in form of Capacitance
- We need to convert these signals to voltage, however, in order to send input to an ADC. This conversion is called signal conditioning.

